

JANUARY
1956

PI NETWORK TANK CIRCUIT, W.I.A. COUNTRIES LIST
HIGH-LEVEL CLIPPING & FILTERING, SINGLE SWITCH CONTROL
RECEIVER CRYSTAL CALIBRATOR, GATED SCREEN MODULATION

Amateur Radio

AMATEURS AND TECHNICIANS!

This is the **BEST SPOT** in Melbourne for . . .

RADIO PARTS AND ACCESSORIES!

Distributors of **ADVANCE, PALEC, TAYLOR, and
UNIVERSITY** Meters and Test Equipment.

And such well-known Radio
Accessories as . . .

- AEGIS products
- TRIMAX products
- A & R products
- FERGUSON products
- ROLA products
- JENSON products
- I.R.C. products
- ALPHA products
- CYLDON products
- B.S.R. products
- MORGANITE Potentiometers
- STENTORIAN Speakers
- STEANE'S Amplifiers
- SUPERSPEED SOLDERS
- GOLDRING products
- CONNOISSEUR products
- EDDYSTONE products
- M.S.P. products
- BELLING-LEE products
- DUCON products
- SIMPLEX products
- BULGIN products
- OAK products
- LEAK Amplifiers
- QUAD Amplifiers
- RADIODRON Valves
- PHILIPS Valves
- BRIMAR Valves
- MONARCH Gramo. Motors
- GARRARD Gramo. Motors
- COLLARO Motors, Pickups



208 LT. LONSDALE ST., MELB.

PHONE: FB 3731 — OPEN SATURDAY MORNINGS!



1/-

"HAM" RADIO SUPPLIERS

(KEN MILLBOURN, PROP.)

Bargains Galore - - Compare These Reduced Prices

NOTE THESE VALVE PRICES

Look at these Bargain Priced NEW VALVES—

1A5 .. 2/6	6K8 .. 15/-	7W7 .. 5/-	VR19 .. 2/6
1B5 .. 2/6	6L7 .. 10/-	12SJ7 .. 10/-	VR21 .. 2/6
1H5 .. 10/-	6L7G 7/6	12SK7 .. 10/-	VR22 .. 2/6
1K4 .. 5/-	6N7 .. 10/-	12SQ7 2/6	VR32 .. 2/6
1K5 .. 10/-	6N8 .. 15/-	12SQ7GT 2/6	VR35 .. 2/6
2A3 .. 10/-	6Q7G .. 5/-	25AC5 10/-	VR38 .. 2/6
2A5 .. 10/-	6R7G .. 10/-	866 .. £1	VR66 .. 2/6
3Q5 .. 5/-	6SC7 .. 10/-	834 .. £1	VR75 15/-
3V4 .. 10/-	6SF7 12/6	884 .. £1	VR102 5/-
6AG7 15/-	6SJ7GT 12/6	954 10/-	VR103 5/-
6B8 .. 15/-	6SK7GT 12/6	955 10/-	VR105 15/-
6C8 .. 7/6	6SS7 12/6	957 10/-	VR122 2/6
6E5 .. 10/-	7A6 .. 5/-	1625 .. £1	VR150 15/-
6F5 .. 7/6	7B8 .. 5/-	5763 25/-	VT50 .. 2/6
6F6 .. 10/-	7C7 .. 2/6	EF50 10/-	VT51 .. 2/6
6K6 .. 7/6	7E6 .. 5/-	U10 2/6	VT52 10/-
6K7G 7/6		VR18 2/6	

Full stocks of New Valves available. Prices on request.

VR90 Voltage Regulator, 15/-.

Following list are ex Disposals, guaranteed—

1K5 .. 5/-	5U4 .. 12/6	6H6 .. 5/-	12A6 .. 10/-
1K7 .. 5/-	6AC7 10/-	6SJ7G 10/-	12K8 .. 10/-
1L4 .. 5/-	6AG5 10/-	6SK7G 10/-	1625 15/-
1S5 .. 10/-	6C5 .. 10/-	6SL7 15/-	CV92 15/-
2X2 .. 10/-	6C6 .. 5/-	6SN7 7/6	EF50 5/-
3A4 .. 5/-	6D6 .. 5/-		

American Murdoch Headphones, 2,000 ohms DC resistance, complete with extension plug 25/- pair

Simulator Sets. Contains two meters 0-20v. and 0-5 Ma., 2 in. square type. Two VR65, one VR135 valves, one vernier dial. Genemotor 11-12v. input, output 480v. at 40 Ma. (conservative rating) and lots of resistors, condensers, etc. £5 each

Inter-Com. Units, English. Contains two valves, transformers, P.M.G. key switch, resistors, etc. To clear 12/6 each

Shielded Cable with two 12-pin Plugs 7/6

Seven-core Cable, not shielded 8d. yard

Co-ax Connectors, Amphenol type, male and female 7/6 pair

Co-ax, indoor type, cotton covered 1/- yard

Co-ax Cable, any length, 50 ohms 1/9 yard

Locktal Sockets 1/6 each

Valve Sockets, ceramic, 8-pin Octal 2/6

Valve Sockets, ceramic, 5-pin 5/-

LARGE STOCK OF CRYSTALS

100 Kc. R.C.A. Crystals £4

1000 Kc. Crystals, DC11 holder, with two pig-tail connect., 35/- Gold Plated Marker and Commercial Crystals, price on request. Delivery in seven days.

Following is a list of Crystal Frequencies available for immediate delivery. £2 each—

2081.2 Kc.	5892.5 Kc.	7028 Kc.	7100 Kc.	8011 Kc.
2103.1 Kc.	6350 Kc.	7028.5 Kc.	7106.7 Kc.	8155.714 Kc.
2112.5 Kc.	6375 Kc.	7032 Kc.	7110 Kc.	8161.538 Kc.
2208.1 Kc.	6450 Kc.	7032.6 Kc.	7120 Kc.	8171.25 Kc.
2218.7 Kc.	6850 Kc.	7035 Kc.	7121 Kc.	8176.923 Kc.
3382.5 Kc.	7004 Kc.	7040 Kc.	7125 Kc.	8182.5 Kc.
3500 Kc.	7005 Kc.	7042.65 Kc.	7126 Kc.	8183.5 Kc.
3535 Kc.	7010 Kc.	7045 Kc.	7130 Kc.	8183.72 Kc.
3600 Kc.	7010.7 Kc.	7047 Kc.	7134 Kc.	
3625 Kc.	7011.5 Kc.	7050 Kc.	7140 Kc.	8320 Kc.
4285 Kc.	7011.75 Kc.	7053.5 Kc.	7145 Kc.	10.511 Mc.
4495 Kc.	7012 Kc.	7063 Kc.	7150 Kc.	10.515 Mc.
5050 Kc.	7016 Kc.	7064 Kc.	7156 Kc.	10.524 Mc.
5300 Kc.	7018 Kc.	7068 Kc.	7162.5 Kc.	10.530 Mc.
5360 Kc.	7021 Kc.	7072 Kc.	7163 Kc.	10.5465 Mc.
5456 Kc.	7021.5 Kc.	7073.5 Kc.	7174 Kc.	10.556 Mc.
5530 Kc.	7021.715 Kc.	7075 Kc.	7175 Kc.	12.803 Mc.
5700 Kc.	7024 Kc.	7077 Kc.	7225 Kc.	12.915 Mc.
5750 Kc.	7025 Kc.	7080 Kc.	8009 Kc.	14.322 Mc.

5A MELVILLE STREET, HAWTHORN, VICTORIA

North Balwyn Tram Passes Corner, near Vogue Theatre.

Phone: WA 6465

Money Orders and Postal Notes payable North Hawthorn P.O. Packing Charge on all goods over 10 lbs. in weight, 5/- extra.

Closing 24th Dec., Re-opening 9th Jan.

AMATEUR RADIO

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA

EDITOR:

T. D. HOGAN, VK3HX.

MANAGING EDITOR:

J. G. MARSLAND, VK3NY.

TECHNICAL EDITOR:

K. E. PINCOTT, VK3AFJ.

TECHNICAL STAFF:

J. C. DUNCAN, VK3VZ.

D. A. NORMAN, VK3UC.

R. S. FISHER, VK3OM.

COMPILATION:

R. W. HIGGINBOTHAM, VK3RN.

CIRCULATION:

I. K. SEWELL, VK3IK.

ADVERTISING REPRESENTATIVE:

BEATRICE TOUZEAU,
96 Collins St., Melbourne, C.I.
Telephone: MF 4505

PRINTERS:

"RICHMOND CHRONICLE,"
Shakespeare St., Richmond, E.I.
Telephone: JB 2419.

MSS. and Magazine Correspondence should be forwarded to the Editor, "Amateur Radio," C.O.R. House, 191 Queen Street, Melbourne, C.I., on or before the 8th of each month.

Subscription rate in Australia is 12/- per annum, in advance (post paid) and A15/- in all other countries.

Wireless Institute of Australia
(Victorian Division) Rooms' Phone
Number is MY 1087.

WI BROADCASTS

All Amateurs are urged to keep these frequencies clear during, and for a period of 15 minutes after, the official Broadcasts.

VK3WI: Sundays, 1130 hours EST, 7146 Kc. and 2000 hours EST 50 and 144 Mc. No frequency checks available from VK3WI. Intrastate working frequency, 7125 Kc.

VK3WI: Sundays, 1130 hours EST, simultaneously on 373 and 7146 Kc., 51,015 and 146.25 Mc. Intrastate working frequency 7135 Kc. Individual frequency checks of Amateur Stations given when VK3WI is on the air.

VK4WI: Sundays, 0900 hours EST, simultaneously on 3560 and 14642 Kc. 3560 Kc. channel is used from 0915 hours to 1015 hours each Sunday for the W.I.A. Country hook-up. No frequency checks available.

VK5WI: Sundays, 1900 hours EAST, on 7146 Kc. Frequency checks are given by VK5MD and VK5WI by arrangements on all bands to 50 Mc.

VK6WI: Sundays, 0930 hours WEST, on 7146 Kc. No frequency checks available.

VK7WI: Sundays, at 1000 hours EST, on 7146 Kc. and 146.5 Mc. No frequency checks are available.

VK8WI: Sundays, 1000 hours EST, simultaneously on 3.5, 7, 14 and 144 Mc. Individual frequency checks of Amateur Stations given when VK8WI is on the air.

Published by the Wireless Institute of Australia,
C.O.R. House, 191 Queen Street,
Melbourne, C.I.

EDITORIAL



DEMOCRACY AT ITS BEST

On the 22nd February, 1857, in London was born a man whose name was destined to become famous both in the military sphere and in every remote part of the globe where mankind lived and flourished. His name was Robert Stephenson Smyth Baden-Powell, better known perhaps under his several nicknames of Ste. (a contraction of his second Christian name, Stephenson, and used mostly by his family); dear old Bathing Towel to his school pals; He of the Big Hat to the Ashanti campaigners; the Wolf that Never Sleeps to his African enemies, the Matabele; and to the world at large as plain but familiar "B-P".

Lord Baden-Powell, as he afterwards became, was a man with outstanding courage, vision and tenacity of purpose. History records details of his Defence of Mafeking during the Boer War in 1899-1900 as one of the outstanding military achievements of all time, yet he was to go on to far greater achievement in completing one of the masterpieces of International organisation—the Boy Scout Movement—a Movement to which he initially gave his spare time and later in life all his time.

Today, despite bitter wars between Nations, the Boy Scout Movement has continued to flourish and expand, carrying on his great teaching—"To train our future men to be level headed, to give fair play to all, to be unselfish, manly and responsible beings". In those few simple words lies a challenge to youth which has been taken up and perpetuated through four generations and will no doubt continue unto eternity.

"Be prepared," he said, and these words became the Scout's Motto. "Train your Scouts as individuals and then harness that individuality for the good of the whole" was his great democratic aim, and to this end he gave his all until his passing on the 8th January, 1941.

In our modern scientific age signalling from the simplest form with lamps or flags to the more complex telegraphic and telephonic systems is one of the primary interests and pursuits of the Boy Scouts. In many countries various Boy Scout Branches have Amateur Radio Transmitting Stations as part of the Scout training in signals. This not only brings the Boy Scout Movement to the forefront in signalling facilities, but proves a worthwhile training ground for those who ultimately choose the radio and electronic field with its wide ramifications as their profession in life. This country will want more and more young people to become interested in the science of radio transmission and reception in its many forms as the population increases and the requirements for technical services in this sphere become greater and greater.

To this end the Wireless Institute of Australia has installed a complete Amateur transmitting and receiving station at the site of the Pan-Pacific Jamboree being held at Clifford Park, Victoria, from 28th December, 1955, to 9th January, 1956, where 16,000 Boy Scouts from the Commonwealth and overseas countries are encamped for one of the greatest Jamborees of all time—a tribute to the great founder of the Movement who lived to see it grow from its inauguration

(Continued on Page 14)

THE CONTENTS

Pi Network Tank Circuit	2	W.I.A. Countries List	12
A Transmitter With Low Harmonic Output—Part Four	5	Amateur Call Signs for September and October	13
High-Level Clipping and Filtering Back Numbers of "Amateur Radio"	8	Fifty Megacycles and Above	14
Integral Crystal Calibrator for Superhet. Receivers	9	Australian V.h.f. Records	14
The Slot Beam	10	DX Activity by VK3AHH	15
Gated Screen Modulation	10	Prediction Chart for January, '56	15
Single Switch Control	10	D.X.C.C. Listing	15
		Federal, QSL, and Divisional Notes	17

Pi Network Tank Circuit

BY K. M. SAXON,* VK7AI

UNTIL recently, the pi network has had little use in Amateur built transmitters, probably because of the difficulties associated with its use in triode amplifiers. But with the trend towards single ended tetrode amplifiers, due in no small measure to the advent of television with its associate t.v.i. of the harmonic variety, the pi network has much to offer from a harmonic reduction point of view, besides affording a simple method of band changing which makes a completely shielded enclosure a relatively simple matter, as access doors do not have to be provided for coil changing. Thus the operator runs no risk of self elimination if he forgets to turn off the high voltage when changing bands.

The main purpose of this article is to describe the writer's final amplifier which uses a pi network. But before doing so, a discussion of the theory of the pi network is desirable.

THEORY OF THE PI NETWORK

The pi network is by no means a new idea. Its main use has been in aerial coupling devices, with some use as a tank circuit in pre-war Amateur portable equipment, etc. It was used in at least one pre-war 5 kw. broadcast transmitter, where its harmonic attenuating abilities were stressed.

At first sight, a circuit diagram using a pi network may appear complex, but it is by no means mysterious to understand.

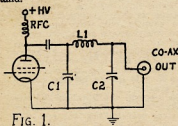


FIG. 1.

The circuit of Fig. 1 shows the network as used as a tank circuit.

C1 and L1 form the tuned circuit elements in much the same way as in a parallel tuned circuit, with the load appearing as a pure resistance across C2.

The loading on the tube is determined by L1 and C2, C1 being used to maintain the circuit at resonance when either of the other two elements is varied. Ideally, both L1 and C2 should be continuously variable as this permits adjusting the load on the tube while maintaining a desired value of Q. For a given Q, C1 would have the same value as in a conventional tank circuit and its value may be determined in the usual way.

If the load connected to the output in Fig. 1 is a pure resistance of known value, a fixed value for either L1 or C2 can be predetermined and the d.c. tube input then adjusted to the desired figure

by varying only one of these two circuit elements. C1 must be variable, of course, to maintain resonance.

If L1 is variable and C2 fixed, the optimum capacity of C2 is such that its reactance is equal to the resistance of the load connected to the output. It happens that when the load resistance is low, of an order of 50-70 ohms as normally used with co-axial cables, this value of capacity at C2 is just about right for maintaining the circuit Q within a reasonable range with most transmitting tubes, particularly those having an estimated plate load impedance of 5,000 ohms.

In actual amplifiers, where the Q may be higher, or with large tubes operated at reduced plate voltage, or two small tubes in parallel, with consequent lowered tube load impedance, the reactance at C2 may be considerably less than the nominal load impedance. Also, if the load is not a pure resistance, C2 has to be adjusted to cancel out the reactance. This may occur with a co-ax link at an aerial coupler unless the coupler correctly matches the link to the aerial.

Sometimes L1 is switched, by means of tapings, to each band and C2 is a continuously variable loading adjustment. This varies the Q of the circuit but is not objectionable, provided the tuning range is the same as is the case with the Amateur bands.

The value of C2 which will provide a given degree of loading on the amplifier depends on several factors. The lower the co-ax output impedance, or the higher the Q of the circuit, the greater

the capacitance required. Also, the higher the load impedance of the tube (given roughly by $500 \frac{E_b}{I_{bma}}$), the smaller the capacitance needed. Typical values of all elements for different bands and tube impedance are given in the accompanying tables. For example, a single 807 with a plate voltage of 600v. at a current of 100 Ma., would have an estimated load impedance of 3,000 ohms. At 7 Mc. C1 = 90 pF., L1 = 6.2 uH., and C2 = 700 pF. For 72 ohm output C2 would be slightly lower.

As in any amplifier to be operated at the higher frequencies, every effort must be made to reduce stray capacitances to a minimum, particularly those in parallel with C1.

Tube output and stray capacitances, plus the variable condenser's own minimum capacitance, add up to a considerable total, making it difficult to keep the circuit Q below 20 or more on 28 Mc. This will reduce the efficiency of the circuit due to heating of the coil, even though the actual tube efficiency may be as high as on the lower frequencies.

Whilst a pi network has very good harmonic attenuation, it will pass frequencies lower than the fundamental with greater ease than a conventional tank. Therefore, the p.a. should not be run as a doubler, nor should it be driven by a doubler unless link coupling is used with two tuned circuits. Also, an aerial coupler is desirable.

One major difficulty is the r.f. choke needed for parallel feed. This must present high impedance on all bands,

TYPICAL OPERATING CONDITIONS AND COMPONENTS FOR PI COUPLED AMPLIFIERS

	Band	Par. 807s	Single 807	813	2E26	
Estimated Plate Load (Ohms)		1,500	2,500	3,000	3,200	4,000
Plate Voltage		600	500	600	800	400
Plate Ma.		200	100	100	125	50
C1 in pF.	3.5	360	210	180	160	135
includes	7.0	180	105	90	50	70
strays	14.0	90	52	45	40	35
(Q = 12)	21.0	60	35	31	28	24
	28.0	45	26	23	20	18
L in uH.	3.5	6.5	10.5	12.5	14.0	15.0
	7.0	3.3	5.3	6.3	7.0	7.8
	14.0	1.5	2.6	3.1	3.5	4.0
	21.0	1.0	1.8	2.0	2.4	2.7
	28.0	0.8	1.3	1.5	1.7	2.0
C2 in pF.	3.5	2,100	1,500	1,400	1,250	1,100
for	7.0	1,050	750	700	630	560
50 Ohm	14.0	540	380	350	310	280
Output	21.0	350	250	230	210	190
	28.0	270	190	175	160	140

All values approximate.

Estimated plate load impedance in ohms = $500 \times \frac{\text{Plate Voltage}}{\text{Plate Current in Ma.}}$

*C/o. Clifton Private Bag, Somerset, Tasmania.

without any series resonances near the bands. A suitable choke is described in the components' list of the transmitter and also in "QST" of May, 1954.

CIRCUIT OF THE TRANSMITTER

The grid circuit employs a multi-band tuner similar to that described in "A.R." for October, 1953. This was found to work as well as a switched or plug-in coil system. The drive is reasonably constant on all bands, being lowest on 14 Mc. where the circuit Q is highest. An 807 operated with about 450v. on its plate can easily supply the required grid drive, even when operated as a doubler. The coupling link should be as short as possible to avoid resonance effects in the link coils which produce heating of the link windings and co-axial cable. As tuning is fairly critical, a vernier dial is recommended.

The tube used is a type 828, though an 813 could easily be substituted, being slightly different physically and requiring no suppressor voltage. Often, an 813 is stable in this circuit, but if necessary, can be easily neutralised as shown by dotted lines in Fig. 2 and described in the A.R.R.L. Handbook.

Neutralisation should not be necessary with an 828, but if it is, proceed as for the 813.

The main tank coil L5 is wound on a 2 1/2" diameter Eddystone ceramic former and is tapped for the various bands. A separate small coil, L4, is used for 28 Mc. This is desirable as it is more readily adjusted to obtain the inductance required for tuning to 30 Mc. with C12 at minimum capacitance. Also, it avoids placing the input capacitance of L5 across C12. (This is even more important when a rotary inductance such as those used in the Command series of transmitters, or the aerial inductance from a BC375 is used for L5.) In addition, L4 can be wound with heavy wire or tubing, which is advantageous considering the higher Q which is unavoidable on 28 Mc.

The coupling condenser C10, and also C11, are 0.0004 uF. units from a BC375 tuning unit (two condensers in each unit). The value of these condensers should not be more than 0.0005-0.001 uF. if the amplifier is to be modulated.

C14 is a standard three section ceramic insulated A.W.A. tuning gang with all sections connected in parallel. C13 is only needed on 3.5 Mc., but should be able to carry considerable current. Four 250 pF. mica condensers in parallel should be satisfactory, or a suitable condenser found in disposals, such as the one rated at 5 amperes at 3 Mc. used in this transmitter.

S1 is a large, ceramic job, also from a tuning unit. A standard Oak switch should be satisfactory if both sections are wired in parallel and it is not rotated when the high voltage is turned on.

C12 presents a problem. One section of a Calstat 120 pF. split-stator condenser was used, but it is rather bulky. The p.a. tuning condenser from a TUE tuning unit should do as its capacitance is 116 pF.

LAYOUT

The amplifier is built on a standard 12" x 17" x 3" chassis with a 12" panel. The grid circuit is enclosed in an 8" x 5" x 3 1/2" aluminium box on the right of the chassis, with M1 above it.

The p.a. tuning condenser, C12, is mounted centrally, directly below the plate meter M2. C14 is mounted at the left, its control dial balancing with that of C12, and S1 is mounted so that it will balance as nearly as possible with the grid meter.

The tube is mounted between the grid enclosure and C12. The 828 needs a cylindrical metal shield about 2" high around its base. Modern practice is to mount the tube socket about an inch above the chassis by means of small pillars. The various by-pass condensers are then connected between the socket pins and lugs mounted on the top of the chassis, with practically zero length leads. This reduces lead inductance to a minimum and keeps all r.f. currents within the plate tank enclosure.

L5 is mounted vertically between C12 and C14, with L4 spanning the gap between C12 and L5. The plate choke, RFC2, is mounted behind C12 and should be kept from metal surfaces in all directions. Keep all earth leads short and r.f. leads as short and heavy as possible. Copper strip 1/2" wide is preferable.

Shielded wire is used for d.c. and heater leads, a piece of co-ax being used for the high voltage. T1 can be mounted under the chassis if it is three inches or less in one direction, otherwise it can be placed at the rear of the chassis where it will require a perforated shield around it. V2 is placed to the rear of the grid compartment, in such a position that it does not obstruct J1.

RFC4 is included as a precautionary measure, to prevent the high voltage appearing on the output circuit in the event of the failure of C10.

TUNING


Initial tuning should be done with reduced voltage. First, tune the grid circuit to obtain about 10 Ma. grid current. It is desirable to check the tuning with a wavemeter and mark each band, but it is practically impossible to tune the wrong band. Next, with C14 at maximum capacitance, C12 is tuned to the resonance dip. If a co-axial line to the aerial is used, C14 is then decreased in capacitance until the desired d.c. input is obtained, maintaining resonance with C12.

If a short co-ax line is used to the aerial coupler, commence as above, and when C12 is resonated, tune the coupler to resonance as indicated by the feeder current or by a rise in the plate current, then adjust the loading by means of C14 as before, checking the coupler tuning a couple of times and keeping C12 resonated.

When a long co-ax line is used to the coupler, it should be accurately matched as per A.R.R.L. Handbook.

Tuning the aerial coupler through resonance should cause the p.a. plate current to rise to a peak then drop away on the other side. If it does not, or if the current should rise when the coupler is detuned, it means that the co-ax line is not matched and adjustment of the number of turns on the link (or its position if a variable link).

(Continued on Page 5)

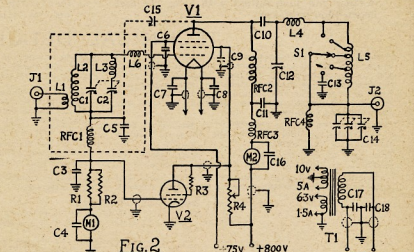


- C1, C2—140 pF. microdeners (ganged).
C3, C8, C7, C9—0.01 uF. mica.
C4, C16—0.002 uF. mica.
C5—500 pF. (or 0.01 uF. if C15 not used).
C6—0.001 uF. 1,000 volt mica.
C7—0.01—0.0005 uF. 2,500 volt mica.
C10—150 pF. 3,000 volts (see text).
C12—0.001 uF. mica (see text).
C14—3 section A.W.A. ceramic tuning gang.
C15—2.10 pF. neutralising condenser, 5,000 volt.
C17, C18—0.005 uF. mica.
R1, R2—30,000 ohms 1 watt.
R3—47 ohms 1 watt.
R4—30,000 ohms 50 watt, adjust. wire wound.
RFC1—15 turns No. 26 gauge enamelled wire, 3 1/2 inches long wound on 1 inch diam. polystyrene rod 6 inches long (see Ref. No. 5).
RFC3—125 mH. 250 Ma. r.f. choke.

- M1—0-50 Ma.
M2—0-250 Ma.
T1—Filament transformer, 10v. at 5 amp.; 6.3v. at 1.5 amp.
S1—1 pole 5 position ceramic rotary (from BC375 tuning unit).
L1—3 turns wound over cold end of L2.
L2—15 turns No. 20, 1 inch long, 1 1/4 inch diam.
L3—8 turns No. 16, 1 inch long, 1 1/4 inch diam.
L4—2 turns No. 16, 1 inch long, 1 1/4 inch diam. angles to each other.
L5—3 turns No. 10, 1 1/4 inch diam., 1 1/4 inch long.
L6—12 turns No. 16, 1 inch long, 1 1/4 inch diam.
L7—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L8—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L9—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L10—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L11—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L12—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L13—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L14—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L15—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L16—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L17—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
L18—2 turns No. 16, 1 inch long, 1 1/4 inch diam.
V1—828 (or 813).
V2—6L6 or 6Y6G.

MODEL "1XA" CRYSTAL MICROPHONE INSERT



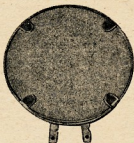AUSTRALIAN MADE — — FOR AUSTRALIAN CONDITIONS



FITTED WITH PLATED REAR SHIELD TO ELIMINATE HUM PICK-UP

- Patented crystal unit guarantees outstanding efficiency and performance.
- Protected against ingress of moisture with approved moisture sealed crystal element.
- Small — compact — lightweight — durable.
- Will not blast from close speaking.
- Precision engineering ensures realistic reproduction and high output with long life and dependable operation.

- The only unit available with a genuine sintered metal filter.
- Good high frequency response ensures excellent speech reproduction.
- Aluminium diaphragm mechanically protected and frequency controlled by "Zephyr" filter.
- Australian made throughout.
- Only carefully selected cements used throughout, to suit Australian climatic conditions.

TECHNICAL DETAILS

Rochelle salt crystal microphones are perhaps the most widely used for all types of service where quality speech and music reproduction at high output levels is a requirement. They are dependable in performance and when fitted with the appropriate "Zephyr" filter, their frequency response may be adjusted to suit any application or requirement.

This crystal microphone requires to be terminated with a high value parallel load of the order of 1 to 5 megohms for best results.

The mass of the moving parts is small, hence the sensitivity is high and a high efficiency is achieved.

Light gauge solder lugs are provided so that excessive heat in soldering will not be transmitted to the crystal element.


When mounted in a microphone cage, it is recommended that the insert be suspended in rubber, to eliminate shock and vibration.

One of the connecting lugs is directly connected to the case and care should be taken to solder the metal shield of the microphone cable to this solder lug, keeping the unscreened portion of the centre conductor as short as possible to eliminate hum pick-up.

All crystal elements are mounted on high grade suspension pillars, being fixed thereto with a good quality cement, thus ensuring stability and long life.

Case $1\frac{1}{2}$ " diameter (rear), $\frac{3}{8}$ " thickness, 1-13/16" overall diameter (front) with filter fitted.

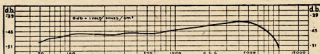Frequency Response = 60-6,500 c.p.s.
Output Level = -45 db (0 db = 1 volt/dyne/cm²)
Impedance = Model 1XA Grid 1 — 5 megohms.



Approximate Frequency Response Curve

AVAILABLE FROM ALL LEADING TRADE HOUSES

ZEPHYR PRODUCTS PTY. LTD.

58 HIGH STREET, GLEN IRIS, VIC.
(Box 2, Armadale P.O., Vic.) Phone: BL 1300

PART FOUR

BY HANS RUCKERT,* VK2AOU

Fig. 5: After passing a shielded mains filter with four button-type 2,000 pF. feed-through ceramic capacitors and a pair of stage layer chokes, the mains voltage reaches four different power supplies. Immediately after switching on the power supplies shown in Fig. 4, the regulated bias voltage is present due to the selenium rectifier used here.

Since the regulator Stabilovolt 40 Ma. $4 \times 70\text{v}$. keeps the current constant, there was a handy way to get the supply for the stand-by relay (RX-TX relay). The other power supply switches all the filaments on, including those of the high voltage rectifier valves. We see again a voltage regulator for 80 Ma. and $4 \times 70\text{v}$.

Note the two current regulators EW and H. They are made of iron wire in a hydrogen atmosphere. One regulates the v.f.o. filament current of 0.7 amp. within 8-24 volts, and the other one keeps the current to the STV280V/80 Ma. constant over a voltage range of 85-225v.

Parallel to the electrolytic capacitors, which are in series, we have to place resistors which have a higher current going through than the leakage current through the capacitors, or we would overload the better one of the two and soon both would blow up.

Figure 6: Two further power supplies are shown on this drawing. We see again fuses on the primary as well as on the secondary side of each power supply, because these are cheaper than replacing burnt out transformers and rectifiers.

The same high voltage power supply is used for the p.a. and modulator final. The 2 x 800v. transformer is capable of 250 Ma. at 800v. d.c. if the mains voltage is not too far down. This is just enough to modulate the 100 watt input carrier to 95% on speech peaks. Running the final with more input would cause negative modulation because the power supply can't stand so much load.

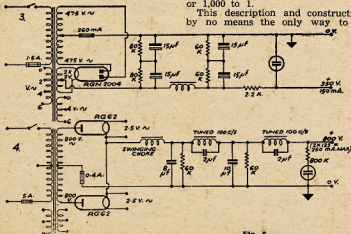


Fig. 6.

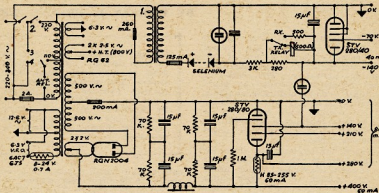


Fig. 5.

The swinging choke was home-made out of an old vibrator transformer by widening the gap at the lamination and rewinding. The output voltage does not vary more than 5% with a load change of 120 to 250 Ma.

The hum filter uses two very small chokes which are tuned with 2 uF. capacitors to the 100 c.p.s. hum frequency.

Re-building of the transmitter last year took two weeks of my holidays to do the mechanical work and many more week-ends for wiring and aligning, plus even more time for special tests of interest.

In spite of poor DX conditions, 350 DX contacts have been enough to work 60 DX countries. The CQ to QSO ratio improved quite a lot, paying off for the effort.

With the receiver in the back yard and reduced sensitivity, the ratio between the fundamental on 14 Mc. and harmonics on 28 and 42 Mc. is as good as 100,000 to 1, and this without the mains and antenna low-pass filter. The old transmitter was not better than 100 or 1,000 to 1.

This description and construction is by no means the only way to solve

t.v.i. problems at the transmitter, but it includes many points which seem to be the logical answers and the writer followed often the methods outlined in "QST" and other publications. Not a penny was spent to re-build the transmitter, all the components were already in the old transmitter or could be found among the bits and pieces one collects after being an Amateur for 25 years.

*25 Berrille Road, Beverly Hills, N.S.W.

(Continued from Page 3)

will probably put matters right. When properly adjusted, it is possible to disconnect the co-ax at J2 without detuning C12 by more than a degree of rotation. The loading can be varied by C14 over a reasonable range without materially affecting the setting of C12, when working into a purely resistive load, after the manner of a variable link in a conventional tank circuit.

The efficiency of the pi network does not suffer by using a tapped or variable inductance (unless the unused portion is self resonant at the operating frequency). No heating of the coil when wound with 18 gauge wire was apparent, even with 100w. input, except a little on 28 Mc. where the Q is higher. Even here it was no greater than when previously using plug-in coils.

I have endeavoured to cover the subject as simply and fully as necessary to ensure a reasonable working knowledge of the circuit. Any queries which may arise, I would be glad to answer, within my capabilities, and I hope that greater interest may be aroused in Australia in a circuit which has become extremely popular overseas.

REFERENCES

- (1) "Practical Applications of Pi Network Tank Circuits," Grammer, "QST," Jan., 1932.
- (2) "Pi Network Design Curves," Grammer, "QST," April, 1932.
- (3) "Pi Network Tank Circuits for High Power," Grammer, "QST," Oct., 1932.
- (4) "High Power Pi Network Amplifier with Parallel Triodes," Bridges, "QST," May, 1954.
- (5) "R.F. Choices for High Power Parallel Feed," Chambers, "QST," May, 1954.

High-Level Clipping and Filtering

New Light on Clipper-Filter Behaviour

BY WARREN B. BRUENE, W0TK

HIGH-LEVEL filtering and "splatter filters" came into use several years ago for the purpose of preventing the radiation of spurious high-frequency sidebands. The high-frequency sidebands generated by overmodulating a plate-modulated amplifier were particularly bad, and the splatter filter^{1,2,3} resulted from the effort to attain a high modulation level without transmitting the splatter so well known in Amateur circles.

However, the explanations given for the operation of these circuits never quite satisfied the writer. While checking the function of the series-diode negative-peak limiter in the "splatter filter," W0JET found that the transmitted bandwidth was less in his transmitter with the diode removed, and he advanced a theory for the reason why. The writer investigated this theory and studied the general problem of high-level clipping and filtering. It is hoped that the following discussion will clear up much of the misunderstanding regarding the operation of splatter filters⁴ and indicate better methods of attaining the desired results.

• This discussion spotlights an inherent defect in the series-diode type of high-level clipper-filter system. The peculiar oscilloscope patterns obtained under certain conditions of modulation are readily explained by the author's analysis, and a better approach to high-level clipping and filtering is described.

cathode and that it appears as an open circuit if its plate gets negative with respect to the cathode. This means that when the voltage at the top end of the modulation transformer secondary, terminal P, swings higher, the diode V1 conducts and the voltage across R (the Class C final) and C will follow the voltage at terminal P. It will actually be just a few volts less due to drop across V1, but this is not significant.


Now, for the purpose of analysis, let the voltage at P swing down to zero instantly. Diode V1 looks like an open circuit because the charge on capacitor C keeps some positive voltage on the cathode of V1 although its plate is at zero potential. Capacitor C discharges through R and the voltage across R (the plate voltage on the Class C final) decays in the usual exponential manner as shown in Fig. 3A. The envelope of the r.f. output for this example is shown in Fig. 3B. If the capacitance of C is increased or the resistance of R is increased, the voltage will drop down at a slower rate. The product RC is known as the time constant of the circuit and this defines the rate of voltage decay.

FREQUENCY EFFECTS


With this background let's see what happens with sine-wave audio modulation. When the audio frequency is very low, the voltage across R follows the voltage at point P over the entire cycle, because the downward voltage swing is so slow that C can discharge fast enough to keep from affecting the voltage across R. As the audio frequency is increased, a frequency is reached where the slope of the downward audio swing is steeper than the slope of the first part of the exponential curve shown in Fig. 3A. This shows up as diagonal clipping on the negative peaks, and it can be observed on an oscilloscope displaying the

r.f. envelope. As the audio frequency is increased, the voltage at terminal P and the voltage on the Class C final changes as shown in Fig. 4 at A, B and C for three different audio frequencies. The corresponding scope patterns are shown in Fig. 4 at D, E and F.

By examining the diagrams in Fig. 4 we can explain a couple of other things that happen with high audio frequency modulation. In Fig. 4B, for example, it is noted that the average plate voltage is higher than the power-supply voltage. Higher average voltage means higher plate current to the Class C final, and this partly explains why the plate current kicks up with modulation when a splatter filter is used. When a steady sine wave is applied as in Fig. 4B, the actual carrier power is increased by

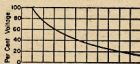

(A)

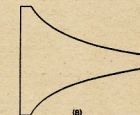

(B)

Fig. 3.—(A) Behaviour of d.c. plate voltage on Class C amplifier when the plate-supply voltage is suddenly reduced to zero. (B) Corresponding oscilloscope pattern of r.f. envelope.

the square of the increase in average plate voltage. Fig. 4B is repeated in Fig. 5 with the dashed line showing the average d.c. plate voltage on the final for this condition of operation. This increased average plate voltage and corresponding carrier power is called "positive carrier shift." The extra carrier power comes from the Class B modulator and is rectified by the diode V1.

Another thing to notice is that the percentage modulation goes down with increasing audio frequency even though the audio signal on the modulator grids is maintained at the same level giving 100 per cent. modulation if diode V1 were shorted out. (It should be noted that we have been discussing conditions where the audio input level would normally give 100 per cent. modulation.) With lower audio signal levels the above results become less pronounced. This circuit thus acts somewhat as a filter in that the high audio frequencies are "attenuated," but this attenuation depends upon amplitude and is less with lower-amplitude audio tones.

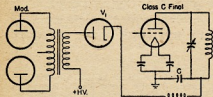


Fig. 1.—Series-diode negative peak limiter or "splatter preventer."

Now let's get to the heart of our subject and examine Fig. 1. This shows a plate-modulated Class C final with a diode in series with the high-voltage supply to the Class C plate circuit. This is the conventional splatter filter circuit with the filter left out. The Class C final tube looks like a pure resistive load to any positive plate voltage. With V1 in the circuit the modulated plate voltage cannot swing the plate voltage negative, so for our analysis we can replace the Class C final amplifier with a resistance as shown in Fig. 2. The other important element of the circuit is the capacitance of the Class C final plate feed to ground. Most of this capacitance is contributed by the plate tank-to-ground by-pass condenser.

Now we can inspect Fig. 2 and see how it performs. First let us note that the diode V1 conducts only when its plate is positive with respect to the

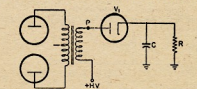


Fig. 2.—Equivalent circuit of Fig. 1, with resistor R replacing the modulating impedance of the Class C amplifier.


* Reprinted from "QST," November, 1951.

1—W. W. Smith, "An Effective Splatter Suppressor," "Radio," October, 1940.


2—Thordarson, "Splatter Chokes and operating instructions."

3—Chicago Transformer Splatter Chokes and operating instructions.

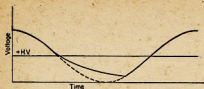4—Howard W. Johnson, "Self-Filtered Peak Clipping," "QST," April, 1948.



(A)

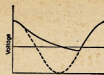

(B)




(C)



(D)



(E)

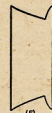

(F)

Fig. 4.—Instantaneous voltage, shown by solid curves in A, B, and C, at the plate of the Class C amplifier at various modulation frequencies when the series diode is used. A—moderately low frequency; B—moderately high frequency; C—very high frequency. The corresponding oscilloscope patterns of the r.f. envelope are shown at D, E, and F.

Fig. 6 shows this carrier shift due to rectification and the "attenuation" in the form of reduced modulation in an actual test case. The carrier shift and per cent. modulation drop will start at correspondingly higher audio frequencies if the 0.007 μ F. capacitor is reduced in value or if the Class C load resistance is reduced.

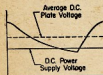


Fig. 5.—Showing how the condition of Fig. 4B results in a change in the average value of d.c. plate voltage, resulting in upward carrier shift.

Incidentally, the writer very carefully checked to see if it made any difference when the diode V1 was placed on the bottom side of the modulation transformer between the Class C final power supply and the modulation transformer secondary.⁴ The difference was always less than $\frac{1}{2}$ db. and did not favor either way consistently.

The other thing to notice is that the modulation is no longer a sine wave and takes on more of a saw-tooth shape. This waveshape contains harmonics of

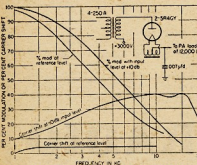


Fig. 6.—Carrier shift and modulation percentage versus modulation frequency in a representative set-up. The curves are referred to the signal-input level, at the grids of the Class B modulators, that gives 100% modulation at 1,000 c.p.s. without the series diode.

the fundamental audio tone so that the actual bandwidth of the r.f. signal is much greater. The extra sidebands generated might be called splatter, although they will not be found to extend across the band as far as the ordinary splatter does. But even though the higher audio frequencies are "attenuated," higher-order harmonics are generated which spread out the signal.

WHERE TO CLIP

In Fig. 7 we have added the low-pass filter to give us the regular splatter filter circuit. Instead of just the simple capacitor C we have the whole low-pass filter. Figuring the time constant—or more correctly, the transient characteristics—of the filter with the load R becomes more complex, but the same type of patterns are observed on the 'scope as those shown in Fig. 4. The "time constant" of the filter varies with the value of m used in the filter design. The writer didn't go very deeply into determining the best value of m, but a few tests indicated that some value around 0.8 was best.

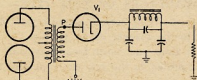


Fig. 7.—Complete splatter filter with series diode and low-pass filter. Resistor R is the modulating impedance of the Class C amplifier.

Now let's try to evaluate the performance of the splatter filter of Fig. 7 compared with the simple high-level filter shown in Fig. 8, which is the same except that the diode is omitted. The splatter filter does reduce splatter to a substantial degree compared with no filter at all, which is attested by its popularity. The writer found in a lab. set-up that using the diode did substantially reduce splatter if the modulators were capable of heavy over-modulation. If their power output cap-

ability was only enough to over-modulate the Class C final slightly, it made no difference whether the diode was used or not.

High-powered modulators, when using a splatter filter, will deliver more sideband power but this extra-heavy modulation is principally effective on the lower voice frequencies, which produce most of the audio power. However, the original research on speech clipping showed that much of the intelligibility contained in speech is in the consonant sounds, which are the higher audio frequencies, and that the vowels or lower voice frequencies can be reduced in amplitude several times without impairing intelligibility. Thus, it is better to use a modulator just capable of 100 per cent. modulation, along with some form of good speech clipping.

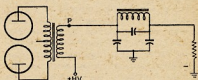


Fig. 8.—Low-pass filter for removing high-frequency components of Class B modulator output and thus preventing splatter. As described in the text, this type of circuit is highly effective when following a Class B modulator adjusted to clip both sides of the wave at or just below the 100% modulation level.

When using the splatter filter the high frequencies, starting from around the cut-off frequency of the filter and going higher, are rectified and cause part of the kicking up of the final plate current meter. However, most of the kicking up is from the heavy modulation of the low frequency positive peaks, which also cause the average d.c. plate voltage to increase on the final. It may be a thrill to see the modulators bluish and the meters kick up, but the value in "getting out" better than a good speech clipper is very doubtful. To "get out" better some form of good speech clipping with modulation limited to just under 100 per cent. is a better solution.

One good place to do speech clipping is right in the plates of the Class B modulators.⁵ This can be done by raising the plate-to-plate load impedance on the Class B modulators until they are not quite capable of 100 per cent. modulation. This can be readily accomplished if a multitap modulation transformer⁶ is used. Another way is to lower the d.c. plate voltage on the Class B modulators (but not the Class C final) until they are just not quite capable of modulating the final 100 per cent. no matter how loudly you yell into the microphone. (Of course, the modulator bias should be reduced also to keep the proper modulator static plate current.) This adjustment should be made with the final loaded in the usual manner or slightly on the light side, because the clipping or plate-overloading level will increase a little in most modulators when the final is loaded more lightly.

Clipping right in the modulator stage reduces the problem of avoiding phase shift of the clipped waves because there

5—Woodrow Smith, "Simplified Speech Clipping," "CQ," May, 1948.

6—Adjustable impedance modulation transformers such as the Multi-tap, Varimatch, Poly-Fedance modulation transformers.

is nothing left to shift phase except the modulation transformer and the high-level filter.⁷ To avoid unnecessary "tipping" of the top of the clipped wave a modulation transformer with good low-frequency response, along with only one section of filter, is recommended. The filter section should be designed with an m of 0.8 or, perhaps better yet, may be a constant-k or simple pi-section filter shown in Fig. 8 doesn't cut off as sharply as the m-section type, but it gives better attenuation farther out, which is more important.

Incidentally, a heavily-clipped wave approaches a square wave in shape and a modulator capable of 100 watts sine-wave output will deliver nearly 200 watts of square-wave output. This helps explain why a transmitter with good speech clipping carries the punch that it does. This isn't hard on the modulator tubes either because their plate efficiency is much higher when passing a clipped wave, so the plate dissipation is nearly the same with either sine-wave or square-wave modulation.

It will be hard on the modulator tubes to run frequency-response tests at 100 per cent. sine-wave modulation up beyond the cut-off frequency of the filter because above cut-off they see essen-

⁷—It is hoped that the effect of phase shift on clipper-filter performance can be discussed in detail in a subsequent article.

tially just the input capacity of the filter, but with voice modulation they can take it. If you want to make life easier for the modulator tubes, put a low-pass filter⁸ up in the front end of the speech amplifier and choose the cut-off frequency of the high-level filter to be a little higher than that of the filter in the front end.

The writer made many tests in the laboratory using all sorts of equipment to test out this theory of high-level clipping and filtering. Also, on-the-air tests at WJBT and WTTK confirm the theory. Many interesting things were discovered during the tests, but space will only allow the basic discussion which has been presented.

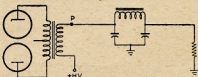


Fig. 8.—Similar to Fig. 8, except that a constant-k filter section replaces the m-derived section of Fig. 8. Formulas for designing both types of sections may be found in The Radio Amateur's Handbook.

In conclusion, the writer wishes to point out again that some good form of speech clipping that clips both the positive and negative audio peaks, followed by a single-section high-level filter, will give about all that can be practically obtained in the way of heavy modulation without splatter.

⁸—Chicago Transformer LPF-1, for example.

Careful choice or adjustment of the modulator plate load impedance to limit the modulator power output is well worth while. For example, when using Class B 810s in a 1-kw. transmitter with 2250 to 2500 volts on them, the plate-to-plate impedance should be about 18,000 ohms instead of 12,000 ohms, to limit the sine-wave output to 500 watts. In addition to better performance, this system is more economical since the cost of several parts is saved and the high voltage peaks on the Class C tank circuit are kept down to normal.

— . . . —

BACK NUMBERS OF "AMATEUR RADIO"

Copies of "A.R.," other than those listed below, are available at the Victorian Division's Rooms, 191 Queen St., Melbourne, at 9d. per copy, plus postage.

1945—October.

1946—February, March, June and November.

1947—January, February, June, July, August, September, November.

1948—March, May and September.

1949—February and March.

1950—July and September.

1951—July.

1952—November and December.

All copies are available for the years 1953, 1954, and 1955.

SPECIAL

BRIGHT STAR RADIO are pleased to announce an addition to their line of Crystals. We are now manufacturing—

VACUUM MOUNTED CRYSTALS

for general communication frequencies in the range 3 to 14 Mc.
Higher frequencies can be supplied.

ADVANTAGES OF THIS TYPE—

- (1) Approximately three times the activity of normal plated crystal due to the absence of air damping.
- (2) Better frequency stability due to the absence of air friction.
- (3) Plating cannot deteriorate with time and cause frequency shift.
- (4) Two or more crystals can be mounted in the one envelope and thus save space.

Price depends on the tolerance and frequency required, and will be quoted upon request.

BRIGHT STAR CRYSTALS may be obtained from the following Interstate firms: Messrs. A. E. Harrold, 123 Charlotte St., Brisbane; Gerard & Goodman Ltd., 192-196 Rundle St., Adelaide; A. G. Healing Ltd., 151 Pirie St., Adelaide; Atkins (W.A.) Ltd., 894 Hay St., Perth; Lawrence & Hanson Electrical Pty. Ltd., 120 Collins St., Hobart; Collins Radio, 409 Lonsdale St., Melbourne; Prices Radio, 5-6 Angel Place, Sydney.

BRIGHT STAR RADIO

46 EASTGATE ST., OAKLEIGH, S.E.12 UM 3387



Integral Crystal Calibrator for Superhet. Receivers

BY S. J. LLOYD,* VK3AST

A BUILT-IN Crystal Calibrator is a useful addition to any communication receiver, but the use of an extra tube for this purpose alone is not always economically possible. In a superhet. receiver, however, the beat frequency oscillator, if suitably modified, can be made to provide calibration points by feeding its harmonics back into the mixer stage.

The average receiver b.f.o. is not suitable as it stands, for two reasons: Firstly, the frequency is usually variable over a small range, and even if not deliberately adjustable, is unlikely to be sufficiently accurate for frequency reference; secondly, its nominal frequency is generally inconvenient for calibration purposes, e.g. 455 or 1600 Kc.

The first defect can be remedied by converting the b.f.o. to a crystal oscillator; a fixed beat frequency is no great disadvantage, and the actual note can be set to any desired pitch during alignment. It can still be varied over a small range, within the i.f. passband, by the receiver tuning. The second disadvantage can be overcome by altering the intermediate frequency, and therefore the beat frequency, to the nearest round figure suitable for calibration purposes. In a receiver with a crystal filter, however, new filter crystals would be required, and it would be better to choose the b.f.o. crystal to suit the i.f., accepting the inconvenience of oddly spaced check points.

monic of a 500 Kc. b.f.o. taken for the beat frequency; in this case a 1500 Kc. crystal could be used in the b.f.o., but the harmonics would be too far apart for accurate calibration.

A double superhet with a second intermediate frequency of the order of 100 Kc. can have a 100 Kc. sub-standard crystal in the b.f.o., giving accurate check points every 100 Kc.

It would also be possible to use such a crystal in receivers with a higher i.f., using the appropriate harmonic (fifth or fifteenth) for the beat frequency; this method has not, however, been tried out, and careful screening would be needed to suppress spurious beats.

If break-through on the altered intermediate frequencies should not be troublesome if a series wavetraps is used, and the screening is adequate.

B.F.O. CIRCUIT

The beat frequency oscillator circuit must be chosen to suit the tube to be used and the activity of the crystal, and should be capable of producing high order harmonics. If the fundamental frequency of the crystal is used for the beat frequency, a tuned circuit is not required; the circuit shown in Fig. 2 has been found suitable for a 500 Kc. crystal and an EF50.

OSCILLATOR INJECTION

The method of coupling the harmonics of the b.f.o. into the mixer stage of the

ably insufficient to cover the altered frequency, and some modification is needed. 455 Kc. transformers can be changed to 500 Kc. by removing turns from the windings, whereas 1600 Kc. transformers will need added parallel capacity to lower them to 1500 Kc. A grid-dip oscillator covering the required range simplifies the conversion.

ADJUSTMENT

With the b.f.o. crystal oscillating, its exact frequency is checked against a standard frequency transmission or reliable frequency meter. If it is not exactly on its nominal frequency, some adjustment is possible by such means as adding extra capacity in parallel, or "loading" the crystal. If it is close to the nominal figure, however, it is simpler to calculate a correction factor to be applied when particular accuracy is required.

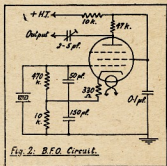


Fig. 2: B.F.O. Circuit.

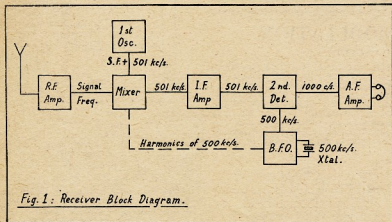


Fig. 1: Receiver Block Diagram.

CHOICE OF I.F.

A receiver intermediate frequency of 455 Kc. can conveniently be altered to 500 Kc. plus or minus the desired audio beat frequency, and an easily obtained 500 Kc. crystal used in the b.f.o.

The crystal fundamental provides the beat note, and the harmonics supply calibration points at intervals of 500 Kc. throughout the tuning range of the receiver.

Similarly, an i.f. of 1600 Kc. can be modified to 1500 Kc., and the third har-

monics will depend on the design of the latter. Simple capacity coupling to the mixer grid, by a small neutralising condenser, is satisfactory; it may be difficult, however, to get adequate injection of harmonics at the h.f. end of the tuning range without overcoupling at the l.f. end. If a spare wafer is available on the band-change switch, a separate coupling condenser for each band is preferable.

I.F. TRANSFORMERS

The range of adjustment provided in the receiver i.f. transformers is prob-

ably insufficient to provide the required beat note with the crystal frequency; e.g. for a beat note of 1000 c.p.s. They are peaked at 1 Kc. above or below the b.f.o. The actual note can be varied by the receiver tuning, as long as it is kept within the i.f. passband.

The coupling between the b.f.o. and the mixer is adjusted to give just enough signal strength on calibration points at the h.f. end of the receiver tuning range.

PERFORMANCE

The arrangement here described has been used for some years in a home-built superhet., using a 500 Kc. crystal in the b.f.o. and an i.f. of 501 Kc. No trouble was experienced with i.f. break-through or spurious beats, and useful calibration points were obtained every 500 Kc. throughout the range from 3.5 to 14 Mc.

An incidental advantage of the system is that the receiver first oscillator can be used to provide a calibrated test signal, as its frequency is always exactly 500 Kc. above the reading of the tuning dial.

THE SLOT BEAM*

BY B. SYKES, G2HCG

Recent developments in Band III television aeriads have led to the combination of the Yagi and skeleton slot aeriads. The result has the advantages of both types without the disadvantages of either.

The fundamental problem with the Yagi is the great reduction in feed point impedance when parasitic elements are added to the simple dipole. This means that when tuning up such an array, it is necessary to adjust the matching at the same time as the elements are tuned to length and the spacing altered. This almost always results in a Yagi with the spacing adjusted for optimum matching rather than optimum gain. Further complications arise when attempts are made to stack Yagis and it is frequently found that two perfectly good four element Yagis giving, say, 8.5 db gain each, flatly refuse to give a further 3.5 db when stacked. The problem again is that of impedance matching. A suitable matching system is of necessity somewhat complicated, both electrically and mechanically.

The search for simplicity and wide bandwidth led to further investigations into the operation of the skeleton slot aerial. The results indicated that parasitic reflector and director elements could be used with the skeleton slot aerial. In addition, the bandwidth was greatly increased by the use of a non-frequency sensitive delta-matching system.

Further examination of the operation of the skeleton slot indicates that the centre portions of the vertical sections

are simply transmission lines feeding two bent dipoles consisting of the horizontal sections and the ends of the vertical sections. The important point to note is that the dipole can "choose" its own length to suit the operating frequency; in other words, the point at which the vertical sides of the skeleton slot cease to be transmission lines and become the ends of a bent dipole is governed by the frequency and not by the size of the aerial. There is, of course, a limit, but the bandwidth can be very wide indeed.

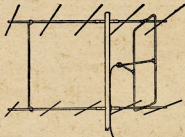


Fig. 1.—A typical six-over-six slot beam. The gain is 12 db over a dipole, the back to front ratio 40 db, and the horizontal beam width 20°.

The skeleton slot, therefore, consists of two stacked end-fed dipoles. The addition of parasitic elements to an end-fed dipole does not alter the feed impedance, but the tuning, i.e., the length of the dipole does alter. Since the dipoles in a skeleton slot array can "choose" their own lengths, it follows


that a skeleton slot can be converted into a stacked Yagi with no matching complications. This is confirmed in practice where such an array may be set-up giving a standing wave ratio of 1.2/1 and reflectors and directors added and tuned for maximum field strength, increasing the forward gain by about 10 db. It is then found that the standing wave ratio has not altered. The age-old problem of matching Yagis and stacked Yagis is therefore solved and all elements can be tuned for maximum radiation with no fear of feed-point impedance changes.

Single Switch Control

BY H. G. WOHLERS,† VK3YV

Making The Old "B" Eliminator Extremely Useful

Many Amateurs today have in their junk pile an old "B" battery eliminator and also several disposals relays of the 24-28 volt high resistance type. These relays can be operated satisfactorily by connecting them in series in banks of 1, 2, 3 or 4 across the output of an old "B" eliminator (tapped type preferable). Sure, it is realised that the regulation of these eliminators is lousy and because of that they are not much good for anything else.

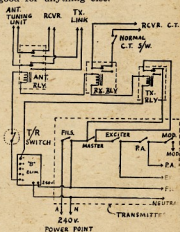

NOTE:—To "NET" WITHOUT ANT. TURN "PA" S/W OFF. TURN "MASTER" S/W ON.

The following is a set-up which has been in use in my shack for at least seven years and has never failed yet. It has given every satisfaction and can be varied in a 100 different ways to suit any Amateur's requirements. After hours of use neither the relays nor the eliminator show any signs of warming up and the original rectifier valve is still in use.


Don't worry about voltages and currents as I have used all sorts and types of relays (except low resistance types) with excellent results. In any case, for those who are interested, it is one good way of making use of disposals relays and old eliminators to operate your station with single switch control.

† 107 Templeton Street, Wangaratta, Vic.

GATED SCREEN MODULATION

BY S. C. BURTON,† VK2AYB

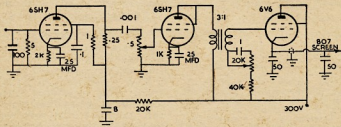Having experimented with clamper and transformer screen modulation, it was found that adjustments were critical, especially when changing bands. With the gated screen, these troubles disappeared. The writer is at present using this method to screen modulate a pair of 807s in parallel and obtaining very pleasing results.




The circuit is simple and sure-fire. The only adjustment is that the loading to the final should be increased to give a small upward kick on the plate meter under modulation. This will necessitate, in most cases, heavy coupling to the antenna coupler.

tion. Suffice to say it will modulate a pair of 807s 80% to 100% at all times.

The loading adjustment seems the most critical adjustment, but once set for any band, should not require altering. Grid drive has some effect on output, but is set at 5 Ma. at this station for 60 watts input.

† 52 Arcadia Street, Penshurst, N.S.W.

RADIOTRON POWER VALVES

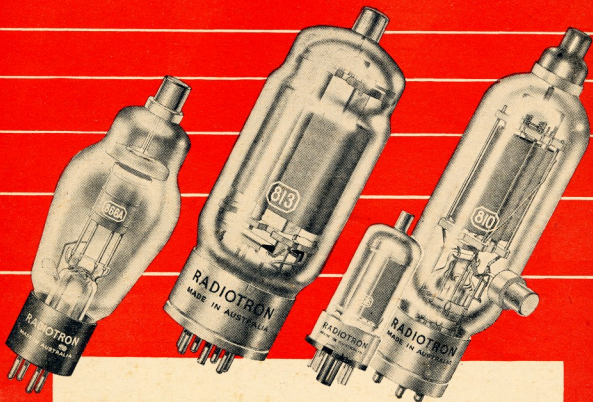

Today's high standards of radio performance are dependant upon the use of first quality components.

Radiotron valves are manufactured to exacting standards which ensure you of the ultimate in performance at all times.

Be sure of the quality and consistency of your signals by using Radiotron Power Valves.

Important: When ordering valves, be sure to mention "Amateur Radio" so that priority can be given to your order.



RADIOTRON

AMALGAMATED WIRELESS VALVE CO. PTY. LTD.

W.I.A. COUNTRIES LIST

Official List for VK DX Contest and the VK DXCC Award

AC3-Sikkim	(22)	HC8-Galapagos Is.	(10)	PK6-Celebes and Molucca		VR1-Gilbert and Ellis Is. &	
AC4-Tibet	(23)	HE-Liechtenstein	(14)	Is.	(28)	Ocean Is.	(31)
AP-Pakistan	(21, 22)	HH-Haiti	(8)	PX-Andorra	(14)	VR2-Fiji Is.	(32)
BV (C3)-Formosa	(24)	II-Domin. Republic	(8)	PY-Brazil	(11)	VR3-Fanning Is. Group	(31)
C (unofficial)-China (23, 24)		HK-Colombia	(9)	PZ1-Nether. Guiana	(9)	VR4-Solomon Is.	(28)
C3-See BV.		HK0-Archipelago of San		SM-Sweden	(14)	VR5-Tonga (Friendly)	
CE-Chile	(24)	Andres and Providen-		SP-Poland	(15)	Is.	(32)
CE7-LU, VK1, VP8		cia	(9)	ST-Anglo-Egyptian		VR6-Pitcairn Is.	(28)
CE7Z, Antarctic (13, 29, 30)		HL-Korea	(25)	Sudan	(34)	VS1-Singapore Is.	(28)
CE0-Easter Island	(12)	HP-Panama	(7)	SU-Egypt	(34)	VS2-Malaya	(28)
CM, CO-Cuba	(8)	HR-Honduras	(7)	SV-Greece	(20)	VS4-Sarawak	(28)
CN2, KT1-Tangier Zone (33)		HS-Siam	(26)	SV-Crete	(20)	VSS-Brunei	(28)
CN8-French Morocco (33)		HV-Vatican City	(15)	SV-Dodecanese	(20)	VS6-Hong Kong	(24)
CP-Bolivia	(10)	HZ-Saudi Arabia	(21)	TA-Turkey	(20)	VS9-Aden & Socotra	(21)
CR4-Cape Verde Is.	(35)	II-Italy	(15)	TF-Iceland	(40)	VS9-Maldives Is.	(22)
CR5-Port. Guinea	(35)	II-Trieste	(15)	TG-Guatemala	(7)	VS9-Sultan. of Oman	(21)
CR5-Principe, Sao		IS, MS4-Italian Somali-		TI-Costa Rica	(7)	VU2-India	(22)
Thome	(36)	land	(37)	TI9-Cocos Is.	(7)	VU2-Laccadive Is.	(22)
CR6-Angola	(36)	IS1-Sardinia	(15)	UA1, 3, 4, 6-European		VU5-Adamam and Nico-	
CR7-Mozambique	(36)	JA, KA-Japan	(25)	R.S.F.S.R.	(15, 16, 17)	bar Is.	(26)
CR8-Cayenne (Port. India)		JY, ZC7-Jordan	(20)	UA9, 0-Asiatic R.S.F.S.R.		XE-Mexico	(6)
CR9-Macao	(22)	JZ0-Netherlands New		(17, 18, 19, 25)		XZ-Burma	(26)
CR10-Port. Timor	(28)	Guinea	(28)	UB5-Ukraine	(16)	YA-Afghanistan	(21)
CT1-Portugal	(14)	K, W-United States of		UC2-White Rus. S.S.R.	(16)	YI-Iraq	(21)
CT2-Azores Is.	(14)	America	(3, 4, 5)	UD6-Azerbaijan	(21)	YJ-See FU8.	
CT3-Madeira Is.	(33)	KA-See JA.		UF6-Georgia	(21)	YK-Syria	(20)
CX-Uruguay	(13)	KA0-Bonin and Volcano		UG6-Armenia	(21)	YN-Nicaragua	(7)
DJ, DL, DM-Germany		Is.	(27)	UH6-Turkoman	(17)	YO-Romania	(20)
(14, 15)		KB6-Baker, Howland and		UI8-Uzbek	(17)	YS-Salvador	(7)
DU-Philippine Is.		Amer. Phoenix Is.	(31)	UJ8-Tadzhik	(17)	YU-Yugoslavia	(15)
EA-Spain	(14)	KC4-Navassa Is.	(8)	UL7-Kazakh	(17)	YV-Venezuela	(9)
EA6-Baleares Is.	(14)	KC5-East. Caroline Is.	(27)	UM8-Kirghiz	(17)	ZB1-Albania	(15)
EA8-Canary Is.	(33)	KC6-West. Caroline Is.	(27)	UN1-Karelo-Finnish Re-		ZB2-Gibraltar	(14)
EA9-Irni	(33)	KG4-Guantanamo Bay (8)		public	(16)	ZC2-See VK1.	
EA8-Rio de Oro	(33)	KG6-Mariana Is.	(27)	UO5-Moldavia	(16)	ZC3-Christmas Is.	(29)
EA8-Span. Morocco	(33)	KG6-Hawaii Is.	(31)	UP2-Lithuania	(15)	ZC4-Cyprus	(20)
EA0-Span. Guinea	(35)	KJ6-Johnston Is.	(31)	UR2-Latvia	(15)	ZC5-Br. North Borneo	(28)
EL-Eire	(14)	KL7-Alaska	(1)	UR2-Estonia	(15)	ZC6-Palestine	(20)
LI-Liberia	(35)	KM6-Midway Is.	(31)	VE, VO-Canada (2, 3, 4, 5)		ZC7-See JY.	
EQ-Iran	(21)	KP4-Puerto Rico	(8)	VE-Australia	(29, 30)	ZD1-Sierra Leone	(35)
ET2-Eritrea	(37)	KP6-Palmyra Group, Jar-		VK1-See CE7Z, LU-Z, VP8.		ZD2-Nigeria	(35, 36)
ET3-Ethiopia	(37)	vis Is.	(31)	VK1, ZC2-Cocos Is.	(29)	ZD3-Gambia	(35)
F-France	(14)	KR6-Ryukyu Is.	(25)	VK1-Heard Is.	(39)	ZD4-Gold Coast, Br. Togo-	
FA-Algeria	(33)	KS4-Swan Is.	(7)	VK1-Macarie Is.	(30)	Land	(35)
FB8-Amsterdam and St.		KS6-Amer. Samoa	(32)	VK9-Norfolk Is.	(32)	ZD6-Nyasaland	(37)
Paul Is.	(39)	KT1-See CN2.		VK9-Papua Territory		ZD7-St. Helena	(36)
FB8-Kerguelen Is.	(39)	KV4-Virgin Is.	(8)	VK9-Territory of New		ZD8-Ascension Is.	(36)
FB8-Madagascar	(39)	KW6-Wake Is.	(31)	Guinea	(28)	ZD9-Tristan da Cunha and	
FC-Corsica	(15)	KX6-Marshall Is.	(31)	VO-See VE.		Gough Is.	(38)
FD-Fren. Togolande	(36)	KZ5-Canal Zone	(7)	VP1-Br. Honduras	(7)	ZE-South. Rhodesia	(38)
FE8-Fr. Cameroons	(36)	LA, LB-Jan Mayen	(40)	VP2-Leeward Is.	(8)	ZK1-Cook Is.	(32)
FF8-Fr. West Africa	(36)	LA, LB-Norway	(14)	VP2-Windward Is.	(8, 9)	ZK2-Niue	(32)
FG-Guadeloupe	(8)	LA, LB-Svalbard	(40)	VP3-Brit. Guiana	(9)	ZL-New Zealand	(32)
FI8-Fr. Indo China	(26)	LU-Argentina	(13)	VP4-Trinidad and To-		ZM6-British Samoa	(32)
FK8-New Caledonia	(32)	LX-Luxembourg	(14)	bago	(9)	ZM7-Tokelau (Union)	
FL8-Fr. Somaliland	(32)	LZ-Bulgaria	(20)	VP5-Cayman Is.	(8)	Is.	(31)
FM-Martinique	(8)	M1-San Marino	(15)	VP5-Juraka	(8)	ZP-Paraguay	(11)
FO8-Clipperton Is.	(7)	MB9-See OE.		VP5-Nurks and Caicos		ZS1, 2, 4, 5, 6-Union of	
FO8-Fr. Oceania	(32)	MP4-Bahrein Is.	(21)	Is.	(8)	South Africa	(38)
FP8-St. Pierre & Miquelon		MP4-Kuwait	(21)	VP6-Barbados	(8)	ZS2-Marion Is.	(38)
Is.	(5)	MP4-Qatar	(21)	VP7-Bahama Is.	(8)	ZS3-St. West Africa	(38)
FQ8-Fren. Equatorial		MP4-Trucial Oman	(21)	VP8-See CE7Z, VK1, LU-Z.		ZS7-Swaziland	(38)
Africa	(36)	MS4-See IS.		VP8-Falkland Is.	(13)	ZS8-Basutoland	(38)
FR7-Reunion Is.	(32)	OA-Peru	(10)	VP8-South Georgia	(13)	ZS8-Bechuanaland	(38)
FU8, YJ-New Hebrides	(39)	OD5-Lebanon	(20)	VP8, LU-Z-South Orkney		ZA-Monaco	(14)
FW8-Wallis and Futuna		OE, MB9-Austria	(15)	Is.	(13)	3V8-Tunisia	(33)
Is.	(32)	OH-Finland	(15)	VP8-St. Sandwich Is.	(13)	4S7-Ceylon	(22)
FY7-Fr. Guiana and		OK-Czechoslovakia	(15)	VP8, LU-Z-South Shetland		4W1-Yemen	(21)
Inini	(9)	ON4-Belgium	(14)	Is.	(13)	4X4-Israel	(20)
G-England	(14)	OQ5, 0-Belgian Congo		VP9-Bermuda Is.	(5)	5A-Libya	(34)
GC-Channel Is.	(14)	OX-Greenland	(36)	VQ1-Zanzibar	(36)	9S4-Saar	(15)
GD-Isle of Man	(14)	OY-Faeroes	(14)	VQ2-Nth. Rhodesia	(36)	—Nabra Is.	(39)
GI-Northern Ireland	(14)	OZ-Denmark	(14)	VQ3-Tanganyika Terr.	(37)	Bhutar	(22)
GM-Scotland	(14)	PA0-Netherlands	(14)	VQ4-Kenya	(37)	—Comoro Is.	(39)
GW-Wales	(14)	PJ2-Neth. West Indies		VQ5-Uganda	(37)	—Fridtjof Nansen L.	(40)
HA-Hungary	(15)	PK1, 2, 3-Java	(28)	VQ6-Br. Somaliland	(37)	Kermadec Is.	(32)
HB1, 9-Switzerland	(14)	PK4-Sumatra	(28)	VQ8-Chagos Is.	(39)	—Mongolia	(23)
HC-Ecuador	(10)	PK5-Nether. Borneo	(28)	VQ8-Mauritius	(39)	Nepal	(22)
				VQ9-Seychelles	(39)	—Wrangel Is.	(19)

AMATEUR CALL SIGNS

FOR MONTH OF SEPTEMBER, 1955

NEW CALL SIGNS

- VK— New South Wales
2MV—C. Welsh, C/o Miss Linsley, 90 Staples St. Kingsgrove.
2AMN—R. D. Martin, 172 Lane St. Broken Hill.
2AOK—J. King, 84 Anderson St. Chetwood.
2ZBF—J. G. Pratt, "Inglewood," R.M.B. 23, Ilabro.
2ZBT—G. T. Adams, 14 Early St., Queenbeyan.
Victoria
3FP—D. Burkitt, Main Rd., Doncaster.
3ADZ—G. E. Delahoy, Eden Park Rd., Whittlesea.
3OLU—L. E. Lloyd, Murray Valley Highway, Nyah South.
3ZAO—R. A. Bailey, 15 Riverside Rd., Ivanhoe.
Queensland
4FF—J. C. Fairweather, Broad St., Labrador.
South Australia
6BJ—B. G. Goode, Yankallilla.
Western Australia
6JJ—B. Bellringer, 97 Grosvenor Road, Mt. Lawley.

CHANGES OF ADDRESS

- VK— New South Wales
2EJ—A. T. Noon, Postal: 29 Oakleigh Rd., Glenhuntly, S.E.9, Victoria.
2EZ—W. G. Spencer, Station: 27 Kardina Rd., Clifton Gardens; Postal: 17a Stanley Ave., Mosman.
2LI—M. F. Moore, 18 Milford St., Randwick.
2QI—C. Bowler, Station: S.S. "Barroona," Postal Address: 25 Castle St., Randwick.
2AJY—J. K. Fullagar (Dr.), 420 Orange Grove Rd., Booker Bay, via Woy Woy.
2ANH—N. H. Hicks, 1 Kitchen St., Oatley.
2AOR—R. B. Digby, 65 Queens Fde., Newport.
2APZ—R. L. Kerdel, 236 Mica St., Broken Hill.
2AQC—R. E. Gummorie, 281 New South Head Rd., Edgecliff.
2AQP—H. F. Powell, 11 Bridge Rd., North Ryde.
2AQS—N. C. Scott, 56 Seventh St., New Lambton, Newcastle.
2ASM—W. C. Clarke, 9 Beacon Ave., Brookvale.
2AWE—R. M. Weston, 127 Anzac Fde., Kensington.
2AXB—E. Curruthers, Station: Flat 16, Hedingley The Esplanade, Elizabeth Bay, Sydney; Postal: Box 1189, G.P.O., Sydney.
2AXS—R. R. Smith, 28 Prospect St., Carlton.
2ZAS—S. D. Russell, 310 Unwins Bridge Rd., Tempe.
Victoria
3DC—D. G. Caldwell, Lot 49, Montgomery Ave., Syndey.
3FI—H. R. Fitzsimmons, 13 Leithen St., Shepparton.
3RL—K. E. Olsson, 6 Kalonga Rd., Nth. Balwyn.
3ARO—R. C. Pulford, St. Helena Rd., Greensborough.
3ASH—R. R. Elkin, 496 Moorabool St., South Geelong.
3ZBH—R. J. Harrison, Railway Pde., Glenroy.
Queensland
4BL—W. A. Easterling, 16 St. Peters St., St. Peters.
4BX—G. J. Walker, 23 Hughes St., Hermit Park.
4CA—D. B. Owen, 24 Anzac Ave., Toowoomba.
4SE—S. E. Molen, C/o, Radio Station 4LG, Cramsie, Longreach.
4TF—R. C. Tow, 5 Hooper St., Boonah.
South Australia
5GE—R. G. Pitts, Flying Doctor Base, Vincent St., Port Augusta.
5SG—S. G. Tonkin, 75 Ways Rd., Hampstead Gardens, Adelaide.

Western Australia

- 6LJ—J. Mead, 68 Alexander St., Wembley.
6WI—Wireless Institute of Australia (W.A. Div.), Station: 110 Edenborough St., Mt. Hawthorn; Postal: Box N1002, G.P.O., Perth.
Tasmania
7FC—F. C. Harland, Station: 12 Wellesley St., South Hobart; Postal: 42 Wellesley St., South Hobart.
7WG—G. Gough, 111 Pottery Rd., Lenah Valley.

Territories

- 9AS—J. A. Whitaker, Station: A.P.C. Oil Exploration Station, Upper Bamu River; Postal: Seismic Five, C/o. A.C.C., Port Moresby.

CANCELLED CALL SIGNS

- VK— New South Wales
2DM—D. W. McDonald.
2XI—C. P. Pickup.
2AGP—C. T. Ralph.
2AIF—J. C. Fairweather. Now VK4FF.
2APN—D. G. Littlejohn.
Victoria
3YA—A. R. Young.
3ACW—C. Welsh. Now VK2MNV.
3AGO—E. C. Slogos.
3AOF—F. P. O'Gwyer.
South Australia
5TM—R. D. Martin. Now VK2AMN.

Territories

- 1DY—G. E. Delahoy. Now VK3ADZ.
9OK—L. J. King. Now VK2AOK.
9FP—P. T. Filmer.

FOR MONTH OF OCTOBER, 1955

NEW CALL SIGNS

- VK— New South Wales
2SD—L. W. N. Squires, Portable, C/o. 27 Fletcher St., Bondi.
2AGE—G. A. Dowse, 6 Bangalow Rd., Ballina.
2AJN—A. J. Myers, 515 Pennant Hills Rd., West Pennant Hills.
2AQA—18 L.A.A. Regt. R.A.A., Chandler St., Kogarah.
2AYA—G. A. Ahlstrom, 21 Melville St., Strathfield.
2ZBB—G. P. Pearson, 17 Esler St., Burwood.
2ZBJ—J. L. Cumming, 8 Sorrie Port, Castlereagh.
2ZBF—B. C. Fleck, 29 Yoolooma St., Griffith 55.
Victoria
3JK—K. H. Kerd, Portable, C/o. Reid St., Wangeratta.
3PD—W. R. Moffatt, 1 Rothsay Ave., Box Hill South.

- 3AJX—A. R. Jarman, 8 Edward St., Horsham.
3AKU—M. J. Doolan, 28 Ekene St., Colac.
3AWV—K. J. Love, 27 Bishop St., Oakleigh.
3AZB—A. W. M. Bueast, 5 Torresdale Rd., Toorak.
3ZBA—W. A. Ferrer, 26 Jeffers St., Noble Park.

Queensland

- 4BB—S. K. Howard, Portable, C/o. 40 Branyan St., Bundaberg.
4BI—H. H. Mullins, Tulley St., Thursday Island.
4ND—N. G. Dangerfield, 23 Graham St., Ayr.
4OC—E. B. Connor, Casowary St., Longreach.
4XD—K. W. Nutt, Station: Mulgrave Rd., Earlville via Cairns; Postal: C/o. Broadcasting Station 4CA, Cairns.

- 5ZAP—G. R. Pope, 16 Seaview Gr., Blair Athol.
Western Australia
6JH—J. W. Hughes, 373 Marine Drive, Geraldton.

- 6MM—G. Miles, 31 The Avenue, Nedlands.
6RB—E. F. Robins, 148 McDonald St., Joondanna Heights.
6ZAF—T. C. Berg, 72 Fourth Ave., Mt. Lawley.

Territories

- 9AB—A. B. Bunting, Station: 3 Mile, Rouna Rd., Port Moresby; Postal: P.O. Box 39, Port Moresby.
9SD—S. D. Sutherland, Station: Cr. Yarra Ave. and Tavus St., Rabaul; Postal: C/o. P.O. Box 55, Rabaul.

CHANGES OF ADDRESS

- VK— New South Wales
2EX—A. H. Outtrim, 30 Boomerang Rd., Springwood.
2IY—T. H. Cahill, C/o. Milparinka P.O.
2JU—J. W. Archibald, 52 Vista St., Sans Souci.
2TJ—J. W. Thompson, 11 Temple St., Stanmore.
2ACK—C. Jeffery, 34 Waitara Pde., Hurstville.
2ALD—R. F. Smith, 47 Denman St., Cronulla.
2AQJ—K. B. Bowyer, Flat 22, Seiffert Centre, Lowe St., Queanbeyan.
2ARI—R. H. H. Roach, 49 Henley Rd., Flemington.
2AWO—W. H. Field, Postal: 10 William St., Double Bay.
2AXD—E. A. Druit, 43 Canal St., Griffith.
2ZAH—W. H. Harder, 148 Blismuth St., Broken Hill.
Victoria
3FO—C. R. Gibson, High St., Maldon.
3ABA—J. O. Bail, 20 Relieve Cres., Box Hill North.
3APK—P. C. Perkins, 29 Richmond St., Geelong East.
3AQK—R. J. Hildebrand, 101 Tambet St., East Bentleigh.
3AVS—M. Strofield, 18 Alexandra Ave., Elsternwick.
3AZC—L. Cunningham, 133 Gordon St., Traralgon.

Queensland

- 4KW—H. S. Dearnese, 16 Harrison St., Mackay.
4RI—R. H. Gordon, Cr. Mark and Gleason Sts., Hermit Park, Townsville.

South Australia

- 5FF—R. F. Farmer, C/o. Mr. C. W. Farmer, 7 Kirkcaldy Rd., Grange.
5KS—R. A. Sedunary, 138 Wellington Rd., Payneham.
5NC—R. G. Clayton, 27 Harrow Gr., Seacombe Gardens.
5RN—D. S. Robertson, Station: Maroonika, Mt. Lofty; Postal: C/o. Physics Dept., Box 4 Canberra, A.C.T.

Western Australia

- 6UF—F. H. Turner, 15 James St., East Cannington.
6ZX—E. E. Greay, Commonwealth Bank of Aus., Leederville.

Tasmania

- 7CF—C. J. Frisby, Flinders St., Brooklyn, Burnie.
7RL—R. V. Bulman, 2 Bond St., Kings Meadows, Launceston.

Territories

- 9WL—J. Widdup, C/o. R.T.C., Sohana, Bougainville.
9DS—D. B. Schroder, C/o. D.C.A., Madang.

CANCELLED CALL SIGNS

- VK— New South Wales
2HJ—J. R. Hamilton (Miss).
2ADM—L. E. Radcliffe.
2ATC—Sydney Technical College.
3AWM—W. R. Moffatt. Now VK3PD.
Queensland
4IB—D. N. Bismire.
4JS—H. W. Gletcher.
Tasmania
7XD—K. F. Nutt. Now VK4XD.
Territories
1TF—T. F. Firmstone.

1956 USHERS IN THE T.V. ERA BRINGING WITH IT MANY PROBLEMS

An ounce of prevention is better than a ton of cure.

Prepare now by carefully shielding and filtering all units and external leads.

GLOR ENGINEERING SERVICES

291A TOORONGA ROAD, MALVERN, S.E.6, VIC. Phone: BY 3774



FIFTY MEGACYCLES AND ABOVE

FREQUENCY CHANGE FOR FIFTY MEGACYCLES BAND

Reminder: 50-54 Mc. Band closes on 31st January, 1956.

See you on 56-60 Mc. Band (now open).

NEW SOUTH WALES

An interesting lecture was given at the November meeting of the V.H.F. Group by Mr. Vandyer on co-axial resonators. Visitors present were JASA, 2EI, 2AID and 5PL. Discussion took place on the new rules applying this year to the Ross Hull Contest. The Group strongly objected to these rules and a letter was sent to all divisions, F.E. and the Federal Contest Committee asking that the rules be withdrawn.

The Fox Hunt held on Sunday, 20th, was won by Bob 2A4 with Perc 2APQ as navigator. Dave 2AWZ was second and 2LG was about half a mile away when the location was announced. The fox, John 2AZO and 2ATO, proved to be a very allusive one. 2ANF and 2ATW were very close to him when he cut the transmission. The fox was in the Richmond area. However, he eluded them and made his final location in the bush, well hidden, near the Yellow Rock Lookout. The fox had had luck with rx trouble and withdrew after lunch.

2ZAY/p made a surprise visit to VK3 with a big signal into Sydney from Wentworth Falls. Dave made quite a number of contacts with the Sydney stations from this location, which was about 50 miles from Sydney and about 3,000 feet high.

50 Mc. has shown increased activity with the summer coming on. There were a couple of openings during the month to VK3 and VK4. The opening of the Ross Hull Contest should bring a lot of activity to this band.—2LG.

VICTORIA

A well attended v.h.f. meeting held an interesting talk by Barry 2ZAG on v.h.f. components at present available in Australia. During his trips interstate, Barry has collected a considerable number of miniature capacitors, trimmers, resistors, etc., which although available, are not widely known to Amateurs. Barry 2APB came along to the meeting to see how 2ZAG is going back to VK2 to take a position with a radio firm. He says it was an opportunity he just couldn't resist and feels it will give him more spare time to spend at Amateur Radio. Barry and his XYL, Heather, were very popular here in VK3 at the hunt, and we hope we'll all be sorry you are leaving us, but we hope to contact you at your new QTH at Cronulla. Bill 3ZAC has been transferred to the Air Force station at Singapore. We'll miss you, too, Bill.


The fox hunt, as usual, provided participants with a very enjoyable night out with a lot of amusing incidents. At the first stop in a lane near the rear of 31D's home in Midvale, Park, the only hound to make a catch was Eric 3ADU. The second stop was in tall-light alley in Elwood. This appears to cause much confusion among the usual frequenters of that particular spot, which was added to as the hounds arrived on the site. All the hounds made several catches during the evening, the most unique, though, was when the fox circled the control station's home and on passing slowly by the front gate, Bob 3OJ ran down the path to meet him. This is the first time that a control station has caught the fox on the run. 3ALZ and 2EAL helped Bob with cross bearings during the evening. The final location was at the home of Bob 3WY, in Burwood, and fox hunters enjoyed meeting Bob and his family and seeing his home. Some made the good luck opportunity by getting a QSL card from him. We are grateful to Bob and Mrs. Anderson for making their home available to the Group and thank them most sincerely.

The first field day of the summer season was a very popular one. Those who went portable were 3GM at Mt. Bunninyong, 3ZBU at the Lake Macquarie Camp, Macquarie, Mt. Macedon, 3ADU at Yurok, 3IBP Mt. Dandenong, 3LN at Mt. Macedon and 3ZAD Mt. Dandenong. Home stations played their part and came on the band in full force, giving portables a never-ceasing string of contacts. During the day there were probably about 50 stations operating; this was very encouraging although we never quite like to hear more stations from portable locations on the next field day, the date of which will be broadcast over 3WV.

The following are the rules governing field days for this season: Scoring will be rated at one point per air line mile in each contact. One contact per band, per field day. The mileage must be agreed to by both parties and will form part of the QSO. QSO will not be complete and points cannot be claimed unless the mileage has been arrived at and agreed to by both parties. Make sure to take an adequate map and compass with you. The hands that may be operated are 144 Mc. and above. The time duration of the field day will be the 24 hours of the Sunday. Both portable and home stations are eligible to participate, but in each contact one station at least must be a portable. Home-to-home station contacts will not be awarded points. Logs to be forwarded to the Secretary of the V.H.F. Group, Bob Stevens, VK3OJ, 17 Jervis Street, Burwood, within fourteen days of the date of the field day. An attractive prize is certainly to be awarded to the winner of each field day for this season.

Evan 3AAP has a new daughter, his first harmonic, 8½ lbs. too; congratulations, OM. 3BQ's son, John, and 3ANK's brother, Don, have both passed their A.O.L.C.P. exam and are awaiting a "Z" call.—Phyl Moncur.

Gippsland stations active during November were 3ZAB, 3QZ, 3TH, 3DI, 3VL, 3ZD and 3TF (Sale). Good conditions on night of 27th November gave 3TY his first Melbourne contact with 3RK, who is the most regular and consistently strong signal heard in Gippsland from the Melbourne area. 3TY uses a 52 and six el. array with screen radiator and a building a new converter. 3ZAB, 3TH and 3ZD are gradually acquiring bits and pieces for new beams and 3TY has been relatively inactive due to arrival of new junior op. 3QZ at Traralgon generally on Sunday nights using about 3w. 3TF, from Yallourn, will not be back on 2 m. until after Xmas.—3ZD.

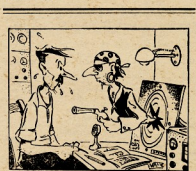

Strike! There must be Pirates on the Band!

WESTERN AUSTRALIA

Most important event of the month was the trip of Bob 6BE and Wally 6ZAA to Albany. 6ZAA's tx and rx for 2 m. were taken and Bob and Wally 6EW provided the 40 and 80 m. links. The week-end was a real hamfest with Wally 6WQ, Bernie 6KJ, Norm 6LT, Harry 6WZ, and Ross 6RD all participating.

The gear was set up at Wally's 6WQ shack and the antenna used was Wally's 12 el. phased array. Input was 50w. on c.w. Signals on Saturday were 550 from Albany. The signal was heard by Rob 6BO, Don 6HK, Ralph 6ZAD and Don 6ZAV. No signals were heard from Perth. On Saturday morning a signal was put into Perth over the 240 mile path, but again Rob could not be heard. On Sunday morning a concerted effort was made to establish a wave contact, but despite reception of 6BE/P signals at 440 in Perth, no Perth station was heard. Whilst two-way contact was not made,

the trip did give all concerned a thrill as it was the most distant check made in W.A. apart from Rolo's efforts to Adelaide.

The thanks of the v.h.f. gang in Perth go to the Albany people for their help and personally I thank Wally, Bernie and Norm for sparing no effort to facilitate our operation. Thanks!

Also promising well for country DX was a phone call to your scribe from Tom Talbot who has applied for his 2 m. call. Tom is in Brunswick, 100 miles from Perth, and hopes to operate on 2 m. The V.H.F. Group will organise an expedition to meet Tom and test the path between Brunswick and Perth. Jack 6EL in Pencilbush has also mentioned an interest in the idea of sending a party to Perth.

Don 6DW, Bruce Rock, made a trip across to Merredin to visit Mal 6MU. Don took a converter and listened for Perth signals. Don has had his 80U in the final succumb and has been on low power since.

In Perth Ron 6ZAR has a strong signal from his 82B. Drive troubles prevent him running much more than 50w. Tom 6ZAP is still having trouble with the tx but has talked his land-lord into joining in the V.H.F. Group's tx hunt. Ralph 6ZAD is happier now with his motor driven antenna. He is planning to install a vertical J, inspired by Roger 6RK. Roger suggested vertical polarisation to erase cross town contacts. Warren 6WJ and Ralph did try it temporarily, but gave the idea away—fortunately! Try halves or turnstiles next time!

288 Mc.: All is quiet here but rumour has it that the W.A. 288 Mc. record will be broken shortly.

Finally, a reminder of real DX. 6 mx operators in the West and some of the 2 licenses monitoring 50 Mc. will be turning it on when 6 mx is open in January. With the improving conditions, the world record of 1,400 miles could be in jeopardy. Who operates on 144 Mc. about 100 miles east of Adelaide?—6ZAA.

AUSTRALIAN V.H.F. RECORDS

Band	Stations	Date	Miles	World Rec'd
50	VK1KL-WTACS/RKH	28/8/47	5385	10500
	VK1HKH-VK1ZP	9/2/52	9929	
	VK6WG-VK2CG	3/1/55	3816	
	VK9BD-ZLJGS	26/12/53	2804	
	VK1M-VK1ZP	30/12/53	2405	
	VK1ZP-VK9BD	31/12/53	2211	
	VK1ZP-VK9BD	31/12/51	1328	1400
144	VK1GL-VK9BO	9/2/52	1328	
	VK1QR-VK1ZP	3/12/52	317	
	VK3GM-3/VK1ZP	9/12/51	106	
288	VK1MT-3/VK9RO-5	13/12/52	106	
	VK1AF-3/VK2AA/P-3	21/3/54	63.8	
	VK6BO-VK6D/W	1/1949	1949	
276	VK1ANW-VK3AKE	11/12/49	81.6	
330	VK1ANW-VK3AXA	16/2/50	81.1	150

The above contacts are best known to date, but what of 4. and 2 m. contacts? Please send FULL details of your best contacts through your Division to F.E., giving particulars of both stations' locations at the time of contact so that your record may be listed above.

EDITORIAL

(Continued from Page 1)

In 1908 to a Movement comprising Boy Scouts, Wolf Cubs, Sea Scouts, Rover Scouts, Queen Scouts, Girl Guides and Brownies. The station is operating under the official Federal call sign of the Wireless Institute of Australia—VK3WIA.

During his early military career in Africa, Baden-Powell observed the native warriors who, because they were the bravest of the brave, held spears in their right hands whilst they shook hands with their left hands. From this grew the traditional left-handed handshake of the Boy Scout. It is therefore with the greatest of pleasure that the Wireless Institute of Australia, as an international democratic representative of the Amateur Transmitting Movement, shakes hands with the International Boy Scouts Association in promoting goodwill amongst Nations.

FEDERAL EXECUTIVE.

DX ACTIVITY BY VK3AHH†

PROPAGATION REPORT

3.5 Mc.: The seasonal increase in noise level naturally affects communications with overseas places. However, conditions to North America and the Pacific Islands continued to be consistent and reasonably reliable, between 0900x

7 Me.: Again, no unusual conditions were observed. Times of band openings were: Europe around 0800z and between 1900z and 2100z; the American Continents and the Far East: 0600-1400z.

14 Mo.: General conditions during the month of November were fair to good. Long path break-throughs to Europe have been observed between 2200 and 0200z. African conditions peaked around 1530-1730z, while the American Continents were well represented between 1200 and 1600z and again around 1930-2300z.

21. Me.: This band provided good conditions to all continents, African conditions were likely to exist between 6500z and 1200z, with Europe around 0900-2400z. South America was workable between 0000z and 0800z, while North

27/28 Me.: Good break-throughs to five continents have been reported. Times were for Europe between 0800 and 1300z, and 2130 to 0200z for the American continents.

NEWS AND NOTES

As usual for this time of the year, **Australian Antarctic Expeditions** are in the headlines! A number of Amateur will again participate in 1956. Our "bon voyage" to the Macquarie Island and Mawson teams is accompanied by welcome-back-home greetings to VKs 1DC, 1HH and 1ZM, who represented Macquarie Island for the last twelve months. The new team will take over around Christmas time. **VK1DA** and **VK1LJ** (ex-7LJ, 3LJ) will be the new call signs.

With apologies to my v.h.f. colleagues, I cannot resist the temptation to mention that "VK4DP is believed to have been heard by two JA stations (one of which was JA1AA) on 50 Mc. at S9" (thanks 4SE). The ball is in the v.h.f. corner now!

Amsterdam Island is represented by FB8ZZ on 14026 Kc. (from W6YY).

14 Mc. phone operation seems to be predominant with **CR7AU**, **CR7CO**, and **CR7DI** (from W6YY).

LUIZY is expected to be active from South Sandwich Islands, beginning late in December or early in January (from BERS195).

Nicobar Islands—VU5—is another one to look forward to (from 5WO).

The **Gough Island** expedition (ZD9AD) had been delayed by bad weather, but has now reached its destination and is active on 14 Mc. c.w. and phone (from 5WO and W6YY).

FD4DB is on 14 Mc. c.w. (from 5WO).
ZLs 2GX and 2CU will soon make
their trip to Kermadec Islands (from
W6YY).

QTHs OF INTEREST

CS3AC—C/o. A.P.O. 406, New York, U.S.A.
CE2CO—P.O. Box 24, Llayllay, Chile.
VQ2SK—Monze Station, Northern Rhodesia.

ACTIVITIES

3.5 Mo.: S.w.l. Dave Jenkin heads this month's list with DU7SV, W5DWT, W6BJU, W7AJS, and W8HOX. 3AHH also heard a number of Ws.

7 Me.: Laurie 2AMB worked XW8AB*, VQ4DW* and heard YU2BO, YU2AC, VS1GX, EA5FI. Syd. 48E reports CT1DJ. Dave Jenkin heard JA9AA and KG6AGT.

14 Me. s.w.: Lyell 2GW: AC5PN*, CE3DZ*, CE4AD*, CN8MM*, CR7CN*, CR9AI*, EA1CP*, EA4CS*, EA5FC*, EA8AF*, EA8BK*, EA8CA*, ET3AH*, FA8AN*, FA8BG*, FA8DA*, FA8IH*

† Hans J. Albrecht, 10 Belgravia Ave., Box Hill

* Call signs and prefix
Z—zero time—G.M.T.

[illegible]

14 Mc. Phone: 2AQJ TICHVY. 3JA: LUCNC;
LUMBU* XZ2SS* FMTWFV* FMTWQV* VY5AO*
OAZA* LUD4MG* KPA4BD* 4RW: ZS8RT
ZS8RT* HIR6R* HIR6R* HIR6R* HIR6R*
VE* HKPC* HP1ER* H1H1B* CS3AC
GM* H1EP* LUM3Z* OAZA* C2C2O*
V1K1AW* VY5BS* HP1ED* FMTWVF* VY3SU*
ZS8QV* ZS8QV* ZS8QV* ZS8QV* ZS8QV*
ZS8QV* ZS8AUJ* ZS8G* CN8MM* VQ4RO*
VQ2SK* VQ2DA* FB8BV* ZS6HO* ZS8AHE*
FA8AY* HK3FV* CQ2BL* EA8AH* CP8AK*
ZS8QV* ZS8QV* ZS8QV* ZS8QV* ZS8QV*
Y5IA* MP4BL* VE* VSSCG* KV4* ZC4RY*
BER8INS* HK3FV* KPA4BD* KR5* OAZA*
VQ4AQ* VK12M* ZK2KN* 4STWM* Dave Jen-

21 Mc.: Neville 2APL: JAs*, KG6*. 3JA:
ZS4PF*, ZS4GN*, 487SN*, VR2*, G*, GD*,
CRAAH*, ZS6GV*, ZS6WS*, ZS6JW*, ZS4GK*,
ZS5PM*, LU3DD*, CE3DY*, ZC4RX*, HC1FS*,
OHINK*, F3DA*, DL*, F3MS*, OH2JC*, ON4-
DB*, OH5PX*, SMTBVO*, 4EW*, GMB3DH*

1SE: JA/K*, VS6*, DL/DJ*, PAOFAB*, Gs*,
ON4*, F8*, SM7AVA*, and VQ3FN, F08AD.
5WO: ZS6JW*, CE3QJ*, KG6*, ZS8FN*,
G3HFD*, G2PU*, DL1JV*, SM5CO*, DL1SD*,
HC1F8*. Dave 3ZAQ (W1A-13003): KR6PI, JA,
VS2DB. Dave Jenkin: KH6S, VS8DE, CE3DY,
VS6AE. KR6RB, KR6CR, CE3QJ, VU5AB.

27/28 Mc.: Les 4XJ worked W0*, W5*, W6*, W7*, W8*, VE4RO*, VE5CT*, VE7EL*, VE7AFA*, VE7VZ*, KH6*, HC1ES*, HC1FS*, HC1KV*, DL1SP*, DL1ZN*, DL1IR*, XE1FU*, JA1ANG*, TG8IW*, BV1U*, and heard TJ1A and YN4CB. John 5HI adds VE7ALC*, JA1ANG*.

G21J*, KH6*, VS2DB*, W8*, VS6CZ*, GW3WO*, KA2NY*, PA0XD*, 5WO spoke to GSSD* and G8TA*. 3ZAQ heard GD3GMH, ON4NC, DL4. Norman BERS11494 listened to YN4CB, W3, W4, W5, W6, W7, KH6, OH, G.

Rare Q8L were received by: 4XJ: HC1KV.
5WO: CX5AF, CE2CO, VP9AK, HP1EH. BERS-
106: PJ2AE, PY2AHW, VP8AZ, VS1GX, XE1UU,
YV1AD, 4S7GE, 4X4GW, 5A2TZ, SM4AWC/MM.

This is the list of last month's contributors:
PJ2AJ, ZLICI, the Northern California DX
Club, and VKs 2ID, 2QL, 2AFE, 2AMB, 2APL,
3HE, 3HL, 3IY, 3JA, 3JE, 3KR, 3PA, 3PG,
3TE, 3WM, 3WQ, 3XO, 3YS, 3ZI, 3ZP, 3ZU,
3ACN, 3AHC, 3AHM, 3ALD, 4HD, 4RW, 4SE,
5BY, 5HI, 5WO, 3ZAT, 3ZBO, and a.w.l's. BERS-
195, WIA-L3019, Dave Jenkin (VK3), and Rod
de Balfour (VK7).

This month, I say thank you to W6YY, and VKs 2GW, 2AMB, 2APL, 2AQJ, 3JA, 3KR, 3YS, 4RW, 4SE, 4XJ, 5HI, 5RK, 5WO, 3ZAQ, and WIA-L3019, BERS195, BERS11494 (VK2), and Dave Jenkin (VK3).

To all readers: Compliments of the Season
with best DX wishes for 1956!

D.X.C.C. LISTING

Listed below are the highest twelve members in each section. New members and those whose totals have been amended will also be shown.

PHONE

Call	Cer. C'tnt- No. ries	Call	Cer. C'tnt- No. ries
VK4FJ	21 181	VK3ATN	26 153
VK3BZ	3 176	VK4KS	9 152
VK4HR	12 176	VK6KW	4 150
VK6RU	2 170	VK3LN	11 141
VK3EE	10 163	VK4RW	23 141
VK3JD	1 155	VK3AWW	14 140

C.W.

Call	Cer. C't-	Call	Cer. C't-
No. ries	No. ries	No. ries	No. ries
VK3BZ ..	6 232	VK3CX ..	26 180
VK3FH ..	15 210	VK4EL ..	9 175
VK4FJ ..	29 206	VK5BY ..	45 172
VK4HR ..	8 200	VK3CN ..	1 163
VK3KB ..	10 200	VK6RU ..	18 161
VK2EO ..	2 183	VK5RX ..	23 159


111

OPEN					
Call		Cer. C'tnt- No. rises	Call		Cer. C'tnt- No. rises
VK3BZ	..	4 231	VK2NS	..	16 195
VK2ACX	..	6 225	VK3HG	..	3 181
VK4FJ	..	32 217	VK4EL	..	10 175
VK4HP	..	3 214	VK6KW	..	13 171

193 V.

Amendments
VK3YS .. 57 112

PREDICTION CHART FOR JAN., 1956

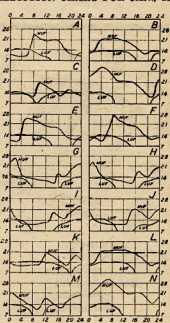

A	-Eastern	Aus. to West.	Europe-Short Route
B	-Eastern	Australia to South Africa.	
C	-Eastern	Aus. to West.	Europe-Long Route
D	-Eastern	Australia to Far East.	
E	-Eastern	Australia to Mediterranean.	
F	-Western	Australia to Western Europe.	
G	-Western	Australia to North U.S.A.	
H	-Western	Australia to North West U.S.A.	
I	-East	Aus. to North	East U.S.A.-Short Route
J	-Western	Australia	to North East U.S.A.
K	-East	Aus. to North	East U.S.A.-Long Route
L	-Western	Australia	to South Africa.
M	-Eastern	Australia	to Central America.
N	-Western	Australia	to Central America.

BOOKS!

BOOKS!

Some useful books to improve your knowledge and save you money:—

- ★ THE SECOND AUDIO ANTHOLOGY—C. G. McProud. 24/- and 1/- postage.
- ★ PHILIPS' VALVE DATA BOOK—10/6 and 9d. postage.
- ★ OSRAM NINE-ONE-TWO PLUS AMPLIFIER MANUAL—7/6 and 9d. postage.
- ★ SINGLE SIDEBAND FOR THE RADIO AMATEUR—25/- and 9d. postage.
- ★ HIGH FIDELITY—Design Construction and Measurements—16/- and 9d. postage.
- ★ R.C.A. RECEIVING TUBE MANUAL—N. J. Harrison. 10/- and 9d. postage.
- ★ MINIWATT, TRANSISTORS AND GERMANIUM DIODES, 2nd Edition. 2/- and 6d. postage.
- ★ AMPLIFIERS (Audio Handbook No. 1)—N. H. Crowhurst. 5/3 and 6d. postage.

We have on display the largest range of Radio & Television books available. Call and inspect them today.

MAIL ORDERS BY RETURN


McGILL'S Authorised Newsagency

Est. 1860

183-185 ELIZABETH STREET, MELBOURNE, C.1, VICTORIA

"The Post Office is opposite"

Phone: MY 1475-6-7

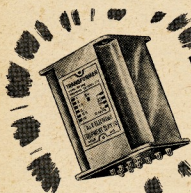

A&R OUTPUT TRANSFORMERS

PERFORMANCE

DEPENDABILITY

APPEARANCE

QUALITY

★ TYPE 921 (921-8: 2 or 8 ohms; 921-15: 3.7 or 15 ohms):

For VALVES:

807, KT66,
etc.

Suitable Conversion

"WILLIAMSON" to U.L.

See "Audio Engineering" of
June, 1952.

20 WATTS: 30-30,000 c.p.s.

Primary: 6,000 ohms.

SCREEN TAPS: 10% of Plate Z.

F.R.: Plus or minus 1 db 10-60,000
c.p.s.

Leakage Inductance:

$\frac{1}{2}$ P/ $\frac{1}{2}$ F: 18 mH. maximum.
Prim/Sec: 20 mH. maximum.

★ TYPE 931 (931-8: 2 or 8 ohms; 931-15: 3.7 or 15 ohms):

For VALVES:

6L6, EL37,
KT66, etc.

See "Radio and Hobbies" of

February, 1953, 17 watts
U.L. Amplifier.

20 WATTS: 30-30,000 c.p.s.

Primary: 4,500 ohms.

SCREEN TAPS: 10% of Plate Z.

F.R.: Plus or minus 1 db 10-60,000
c.p.s.

Leakage Inductance:

$\frac{1}{2}$ P/ $\frac{1}{2}$ F: 15 mH. Maximum.
Prim/Sec: 15 mH. maximum.

★ Ultra Linear Output Type—

Type 916—12 watts.
Prim.: 8,500 ohms p.p. (with
screen taps).

Sec.: 916-8: 2 or 8 ohms;
916-15: 3.7 or 15 ohms.

Type 940—12 watts.

Prim.: 8,900 ohms p.p.

Sec.: 2, 8, 12.5 15 ohms.

Response: 10-50,000 c.p.s.

Valves: 6V6, 6BW6, KT61,
EL84, etc.

10% Screen Taps.

★ For Mullard "5-10" Amplifier

Type 2505—12 watts.

Prim.: 6,000 ohms c.t.

Sec.: As below.

Response: 10-50,000 c.p.s.

Type 2505—8 watts.

For 2 or 8 ohms Secondary.

Type 2505—15 watts.
For 3.7 or 15 ohms Secondary.

MANUFACTURED BY—

A & R ELECTRONIC EQUIPMENT CO. PTY. LTD.

378 ST. KILDA ROAD, MELBOURNE, VIC.

Details from these EXCLUSIVE A & R DISTRIBUTORS!

QUEENSLAND:

A. E. Harrold,
123 Charlotte St., Bris.

TASMANIA:

Homercrafts Pty. Ltd.,
220 Elizabeth St., Hobart

WEST. AUST.:

A. J. Wyle Pty. Ltd.,
1011 Hay St., Perth.

SYDNEY — N.S.W.:

United Radio Distribu-
tors P/L 175 Philip St.

Homercrafts Pty. Ltd.,
100 Clarence Street.

SOUTH AUST.:

Gerard & Good-
man Ltd.,

196 Rundle St.,
Adelaide.

MELBOURNE & VIC.:

J. H. Magrath & Co.
Pty. Ltd.

Motor Spares Ltd.
Radio Parts Pty. Ltd.

Warburton Frankl Ltd.

FEDERAL, QSL, and DIVISIONAL NOTES

FEDERAL THE NEW YEAR

Once again the Federal Council and the Federal Executive of the Institute desire to wish all members Happy and Prosperous New Year.

It is appropriate at this festive season to give a few moments' thought to those whose work and efforts have kept our Institute functioning. Many play a part, and a special vote of thanks and good wishes for the future goes out to the Magazine Committee, Federal Contest Committee, QSL Managers, Correspondents, Traffic Officers and the others who, behind the scenes, make the smooth running of the I.R.S.

1956 promises much in electronics with Television on the immediate horizon. However, with experience from the past to guide its decisions, the W.I.A. can look with confidence to the future.

FEDERAL STATION VK3WIA

Members will have noted that the Federal Station VK3WIA belongs to the Post-Pacific Scout Jamboree at Clifford Park, near Melbourne.

It is intended by Federal Executive to have this station in operation during the coming year.

Regular broadcasts, disseminating news to all Divisions, are proposed. These will be given by members of Executive and will cover topics of a Federal character. In this way, all will be kept informed of the activities and problems of Executive and its kindred bodies at first hand.

FED. CONTEST COMMITTEE

A letter was received concerning the issue of Certificates for Awards made to winners of past Contests from which it appears that many VK/LZ Certificates have not been sent. It was resolved by the Committee that as soon as time permits the omissions would be rectified.

To assist the Committee, it is asked of contestants who were due for Awards in ALL the Contests run by W.I.A. up to the end of 1954, that they notify the Committee immediately, Box 1254K, G.P.O., Adelaide, together with the details of Contest Awards.

The question of having a sub-committee conference at the Easter Convention, if one is to be held, was discussed at some length and no decision was reached. However, the Divisions regarding the framing of rules for the various contests, it would seem that such a conference will be the only means of arriving at some unanimity.

The value of comments received, along with logs submitted by contestants regarding rules, conduct of the contest, etc., brought serious discussion and it was agreed that these comments should be the true guide to any alterations. It was felt that those who submitted logs were the interested parties. However, where there is a definite policy directive, the Committee has no option but to follow that policy until such time as the Council either repeals it or frames some other policy.

Photographs of the Ross Hull Memorial Trophy have been received by the Chairman and are to be publicly inscribed and sent to the previous winners. A letter will be forwarded to each winner before his copy is sent. Those who receive these very fine plaques will certainly congratulate Federal Executive on their foresight when they agreed to a request from the Contest Committee for permission to have them done.

FEDERAL QSL BUREAU

RAY JONES, VK3RJ, MANAGER

Tom Leitler, VK3ZL, Postmaster at Alice Springs, NT, advises that he will be getting on 1400 c.w. twice daily for the benefit of overseas stations desiring the contact with Northern Territory for the W.A.V.K.C.A. awards. Tom will get on at 0900 and 2100 G.M.T. All contacts will receive a QSL via the Bureau.

VK3RJ will appear on 50 Mc. as soon as he constructs a tx for that band. He is still in the building process.

Interesting cards sighted during November are those of YAIAM, of Kabul, Afghanistan, F777 of Cayenne; French Guiana, and AC4YN, of Tibet. The latter card confirmed a QSO with VK3RJ on 27th August 1954.

Eskil Eriksson, SM4AWC/MM about M.S. "Mangarella" would appreciate a visit from

any local Amateurs while his ship is in various VK ports. He recently was at Melbourne, Adelaide, Port Pirie and Burnie. The ship runs between VK and the West Coast of U.S.A. Eskil operates 14 Mc. c.w. during the voyage. His QSL shows a nice picture of the ship.

Mick Russell-Clarke (ex-VK4IC, of Willis Island, and now resident in VK3 land) advises that he hopes to have his QSL ready for distribution in the near future. During his sojourn of 12 months at Willis Island 400 miles East of Cairns, Mick kept VK3C on the air almost daily, using c.w. and phone.

Any VK who worked VP8AZ and did not obtain a QSL card, can apply again to Mr. Faulkner, 13 Lovatt St., Newport, Pagnell, Bucks, England. VP8AZ operated from Graham Land, Antarctica.

FEDERAL AWARDS

W.A.V.K.C.A. AWARD

Additional Certificate, No. 19, has been issued to J. P. Grubbe, WRT.

OFFICIAL COUNTRIES LIST

Elsewhere in this journal will be found the official countries list as at this date. The list is made up in alphabetical order of prefixes and zone numbers are also listed.

ADDITIONAL COUNTRY

Kermadec Island, a dependency of New Zealand, has been declared to be a new country, effective 1/1/55. It would appear that Laos, Cambodia and Viet Nam will be declared separate countries by the time this reaches the press.

—G. Weynton, VK3XU, Awards Manager.

VICTORIA

STATE CONVENTION

Those who attended the State Convention at Bendigo had a very enjoyable week-end, some renewing old acquaintances, others making acquaintances with fellow Amateurs who up till that time had only been voices. Approximately fifty-three attended the Convention; this was not as large a crowd as usual and was a little disappointing for the organisers. After the dinner and the departure of the ladies to the pictures, the OMs got down to the business of the Convention.

There were six items on the agenda and these were apparently very fully discussed as they were still discussing item 5, "White Hills," when the ladies returned to rejoin them at supper. After supper a film from the Monsanto Chemical Co. on their latest developments in the chemical field was shown. This film was very interesting, but it was also very late by the time everyone got to bed.

However, a State Convention only comes once a year. Those who slept at the hotel got a good night's rest, but those who camped at that very picturesque park, "White Hills," know exactly what sort of a noise a peacock makes all night long.

The first item on the programme on Sunday was a 30 min. hunt on 2 mcs. For some of the competitors this provided a scenic tour of Bendigo over mine shafts and "molecular" traps as someone's harp was blown down those traps of rubble to be seen everywhere around Bendigo. The tx was finally located by Laurie 3ALY at Lightning Hill, near Eaglehawk. Those who located the tx there were rewarded for their efforts by a wonderful panorama of the Bendigo district which could be viewed from a lookout at Lightning Hill.

Then followed another tx hunt, this time on 30 metres. This was a really difficult hunt. After traversing some bush track in heavily wooded country, the tx was located firstly by Don 3ALQ deep in the scrub in the vicinity of One Tree Hill, nearly an hour after the signal had come on the air. While these hunts were being run, a bush tour of Bendigo, as alternative entertainment, was enjoyed by others.

After lunch all gathered at the White Hills Gardens where there were events for all. Two frequency guessing competitions were won by Bill 3AMR and Associate and by a 3ALQ, a nail driving competition for ladies was the next on the programme and this was won by Marj (Mrs. 3ALY), followed by a "cupping" or "ericklet pitch" which was won by Alma (Mrs. 3AMR), and a treasure hunt for the children, won by the President 3TA's barnyard.

A grand week-end altogether. We thoroughly enjoyed every moment of it, our only regret

was that there were not more there to enjoy it with us and reward Neville 3ACN for his colossal job in organising the Convention, and Pat, his fiancée, who was a charming little hostess to the ladies.

GENERAL ITEMS

The A.O.C.F. Class got away to a good start with twenty-two pupils attending on the first night, however there are still a few vacancies for anyone desiring to do the course. Yours truly joined in the struggle once again, pretty tough on poor old "teach" though, he has to leave out most of his appropriate little stories with a female in the class.

The best item of news for the month was the announcement of the engagement of life member and councillor, Jack Duncan, 3VZ, to Miss Phyl Mumme. They plan to marry early in the New Year. Congratulations and best wishes are extended to you both, Jack and Phyl. (Looks as though this Fox has been running with the hounds.—Ed.)

Low Drift Crystals FOR AMATEUR BANDS

ACCURACY 0.02% OF
STATED FREQUENCY

3.5 Mc. and 7 Mc.

Unmounted £2 0 0

Mounted £2 10 0


12.5 and 14 Mc. Fundamental
Crystals, "Low Drift,"
Mounted only, £5.

THESE PRICES DO NOT
INCLUDE SALES TAX.

Spot Frequency Crystals
Prices on Application.

Regrinds £1 0 0

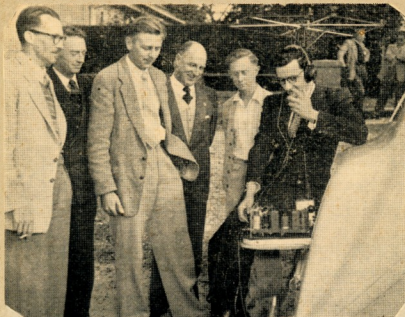MAXWELL HOWDEN
15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA



Calling CQ at State Convention (Bendigo). Left to right: 3AFJ, 3AKW, 3ACN, 3ZS, 3AWC, 3ATK.

For the holiday week-end at the end of January, a group of Amateurs and their families are going to Portarlington to enjoy camping, Amateur Radio, the seaside and perhaps a little fishing. If you are interested in these things, come along and join us. For further particulars get in touch with Mrs. 3LN (PU 6230).

The Institute activities wound up for 1955 with a family night in a real Xmas spirit. This was in place of the general meeting and OMs, XYLs and harmonics enjoyed a very excellent selection of films. The children all received a Xmas novelty and supper was enjoyed by all. The President, Gordon 3TF, extended to members and their families, Xmas

greetings and best wishes for the coming New Year.

SOUTH WESTERN ZONE CONVENTION

The activities this month have been very numerous with the Convention held in Colac on 12th and 13th November. Several chaps worked mobile coming down, but conditions did not favour us on 29 mcs. 144 Mc was extra good as Tony 3ZAZ and his XYL were transmitting whilst mobile to 3AGV in Colac, although Pauline had to do all the driving.

On arrival we were greeted at 3AGV's QTH and received hotel bookings for the evenings, or should I say mornings' sleep, as that is how it usually turns out, as John 3AGD and Kevin 3AKR will agree.

Those present at the dinner were as follows: Bob 3IC, Harry 3XI, Tony 3ZAZ and XYL Pauline, John 3AGD, Gordon 3AGV, Brian 3ZBS, Merv 3AKU, Ed 3AEM, Bill 3AWZ, Ron 3KX, Dod 3KJ, 3AXU, Leigh 3II, Reg 3AFR, Bill Wines and Jack 3ALP. We were very fortunate in having as our guest WIDKC, Earl Whiddon, from Boston, Mass., U.S.A.

The Convention was officially opened at the dinner by His Worship the Mayor of Colac, Cr. D. Stalker, 3KJ. We trust that this event may tend to increase public interest in the affairs of Amateur Radio.

The M.C. at the dinner was Chris 3AXU who has not been in the zone a great time, but did an excellent job along with Gordon 3AGV who had all the responsibilities.

After the dinner, Chris 3AXU brought the tape recorder with him and we heard a very good lecture by Dr. Grote Reber on Radio Astronomy, which was most interesting. Following this we had another lecture on the tape, this was on Atomic Energy by Professor Baxter, which also was most interesting.

After the conclusion of these lectures, 3II had his projector and he presented a few films including the beautiful coronation film. Leigh, you had better bring it to the Warrnambool Convention in March.

Supper was served later in the evening in the hotel dining room. After supper, we migrated to our rooms for some shut eye, but room 12 did not go QRT until about 2:30 a.m. as Harry 3XI, Bill Wines, John 3AGD, Tony 3ZAZ started to re-build a modulator of a Type 3 while awaiting the late arrival of Kevin 3AKR, who was working mobile on his way down from Westmere. He arrived at 12:45 a.m. and took over the modulator building.

**NO! WE HAVEN'T
BEEN HIDING
OUR LIGHT UNDER
A BUSHELL!**



You may think that the TRIMAX Range of components is decidedly limited, but nothing is further from the truth! We do not seek to present a full range in our advertising, but rather prefer to offer you a most comprehensive catalogue of selected components, from Audio and Power Transformers to Electrical Connectors. The December, 1954, issue of the TRIMAX CATALOGUE saves you leafing through old magazines! So . . . SEND FOR IT TODAY!

TRIMAX TRANSFORMERS

PTY.
LTD.

Corner CHARLES ST. & WILLIAMS RD., NORTH COBURG, VIC. — FL 1203

N.S.W.: University Graham
Instruments Pty. Ltd.

STH. AUST.: C. N. Muller
Pty. Ltd.

QLD.: C. A. Pearce & Co.
Pty. Ltd.

WEST AUS.: R. D. Benjamin

Page 19

Amateur Radio, January, 1956

Homecrafts

PTY LTD.

AMATEURS'
BARGAIN
★ CENTRE ★

Test Equipment for Immediate Delivery

TAYLOR R.C. OSCILLATOR

TYPE 191A

Covers Audio Ranges from
10 c.p.s. to 100,000 c.p.s.

Fine and Coarse Attenuators.
Sine or Square Wave Output.
£56/9/3 plus tax.

ADVANCE R.C. OSCILLATOR

TYPE H-1

Covers Audio Ranges from
10 c.p.s. to 50,000 c.p.s.

Sine or Square Wave Output.
£41/10/- plus tax.

ADVANCE SIG. GENERATOR

TYPE E-2

Covers Radio Frequencies from
100 Kc. to 100 Mc.

External or Internal Modulation
£46/8/6 plus tax.

ADVANCE SIG. GENERATOR

TYPE Q-1

Covers U.H. Frequencies from
7.5 Mc. to 250 Mc.

£74/12/- plus tax.

TAYLOR MUTUAL CONDUCTANCE VALVE CHECKER

TYPE 45C

Will check every known type
of Electronic Valve.

£49/3/6 plus tax.

PATON VCT-3 VALVE CHECKER AND MULTIMETER

£46/15/- plus tax.

PATON ET4 VALVE CHECKER

£37 plus tax.

PATON TV-M ELECTRONIC MULTIMETER

£46/17/6 plus tax.

PATON M32 MULTIMETER

£16/16/- plus tax.

PATON M42 MULTIMETER

£28/17/6 plus tax.

UNIVERSITY SIG. TRACER AND V.T. MULTIMETER

TYPE A.S.T.

£60 plus tax.

UNIVERSITY VALVE AND CIRCUIT TESTER

TYPE T.S.T.

£58 plus tax.

UNIVERSITY MULTIMETER

TYPE MVA-2

£16/16/- plus tax.

All Test Equipment Available on Hire Purchase

290 LONSDALE STREET, MELBOURNE


FB 3711



Società per
Azioni Geloso,
Milan.



Belling & Lee Ltd.
Enfield,
Middlesex

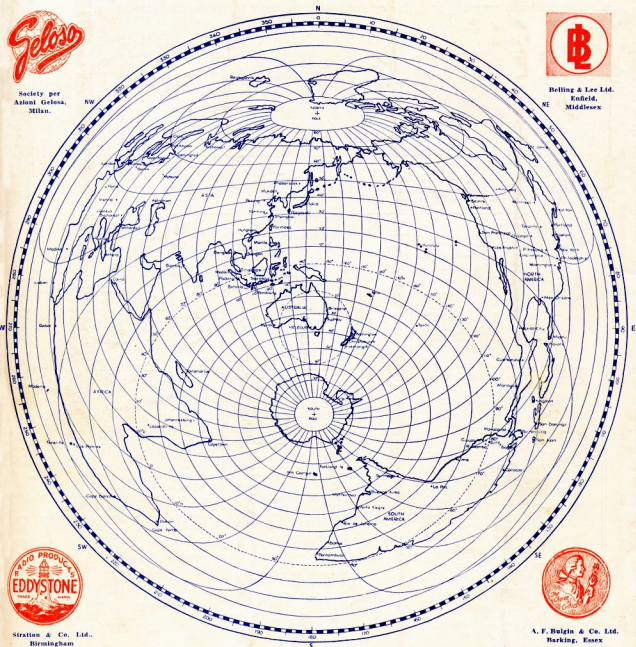

Stratton & Co. Ltd.,
Birmingham



A. F. Bugin & Co. Ltd.
Barking, Essex

This Great Circle Bearing Map
of the World is another service
to Amateur Radio Operators
from R. H. Cunningham Pty.
Ltd.

R. H. CUNNINGHAM PTY. LTD.
118 WATTLETREE ROAD, ARMADALE, S.E.3, VIC.
and 184 VICTORIA ROAD, DRUMMOYNE, N.S.W.